


Memory Interfacing

Ex Design an 8085 system

8K EPROM using 4KB chips and 16KB RAM using 8KB chips

When μP generates an address only the chip whose addr is given should be selected.

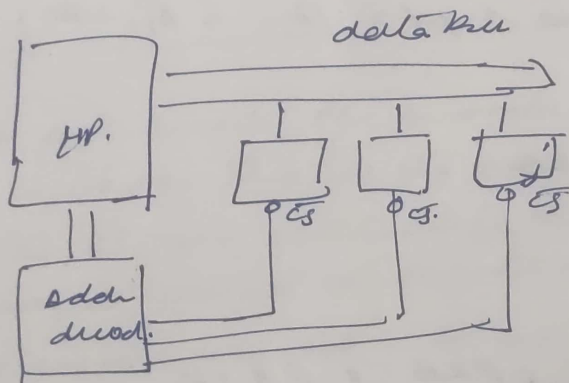① When addr given by μP goes to decoder the decoder selects the chip and the data from the data bus enters into the selected chip



working at 3MHz.

Ex Design an 8085 system with 8K EPROM using 4KB chips and 16KB RAM using 8KB chips

Memory calculation

EPROM : Required - 8KB
Available - 4KB.

No of chips - 2 require

Size of single chip - 4KB. $= 4 \times 1KB.$

$$= 2^2 \times 2^{10}$$

$$= 2^{12}$$

\therefore 12 address lines reqd.

Size of the address bus can be used to calculate the size of the memory.

If n address lines then size of memory is 2^n .

Also from size of memory we can find no. of address lines.

μP has 16 address lines but all are not used to go to the chip. Only the used address lines need to go to the chip.

In this case the size of the chip given = 4KB.

\therefore Address lines used = 12. $= A_{11} - A_0$

RAM

Required = 16 KB

Available = 8 KB.

No. of chips = 2.

Size of single chip = 8 KB $= 8 \times 1K$

$$2^3 \times 2^{10} = 2^{13}$$

\therefore 13 address lines used $= A_{12} - A_0$.

\therefore Address lines used in EPROM = 11

" " " for RAM = 13.

Chip	Addr Bus																Addr Mem
	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
ROM1																	
Begins	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0000H.
Ends.	0	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	0FFFH.
EPROM2																	
Begins	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	1000H.
	0	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1FFFH.
RAM1																	
	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	2000H.
	0	0	1	1	1	1	1	1	1	1	1	1	1	1	1	1	3FFFH.
RAM2																	
	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	4000H.
	0	1	0	1	1	1	1	1	1	1	1	1	1	1	1	1	5FFFH.

Whenever FIP reset PC becomes 0000. So the 1st addr is 0000. This is the addr of the BIOS to load the OS and initialize the chips. This BIOS program is stored at location 0000. So this program should never be lost. So we have to store reset EPROM and not with RAM.

BIOS program cannot be stored in RAM. as it can be erased and lost. In fact in EPROM and not in RAM.

To calculate EPROM 1 ending addr :-

3 addr lines are going in the chip.

When you're calculating the ending addr. you are adding the addr lines calculated for EPROM to 0000H. Since last 4 bits are not there

the 15th 14th 13th 12th - 0000 will be carried forward

Also line A₁₁ - has a 0 + 1 = 1

If A₁₁ start was 1 + 1 = 10 So 0 1

0000 - 0FFF 4KB
 + 1000 - 1FFF 4KB } 8KB

So 2000 - 3FFF will be 8KB.

RAM \rightarrow 2000 - 3FFF.

Next 8K \rightarrow ~~3000~~ 4000 - 5FFF

Eg for carry

Suppose it was 16 KB chip it should.

$$16 \times 1K = 2^4 \times 2^{10} = 14 \text{ lines.}$$

\downarrow

2000 - Start address.

0010	0000	0000	0000
11	1111	1111	1111
0101	1111	1111	1111 — 5FFF

Map is a plan.

Circuit for the implementation. is as follows

0000 - 0FFF 4KB
 +000 - 1FFF 4KB } 8KB

So 2000 - 3FFF will be 8KB.

RAM \rightarrow 2000 - 3FFF.

Next 8K \rightarrow ~~30~~ 4000 - 5FFF

Eg for carry

Suppose it was 16 KB chip it should.

$$16 \times 1K = 2^4 \times 2^{10} = 14 \text{ lines.}$$


\downarrow

2000 - Start address.

0010	0000	0000	0000
11	1111	1111	1111
0101	1111	1111	1111 — 5FFF

Map is a plan.

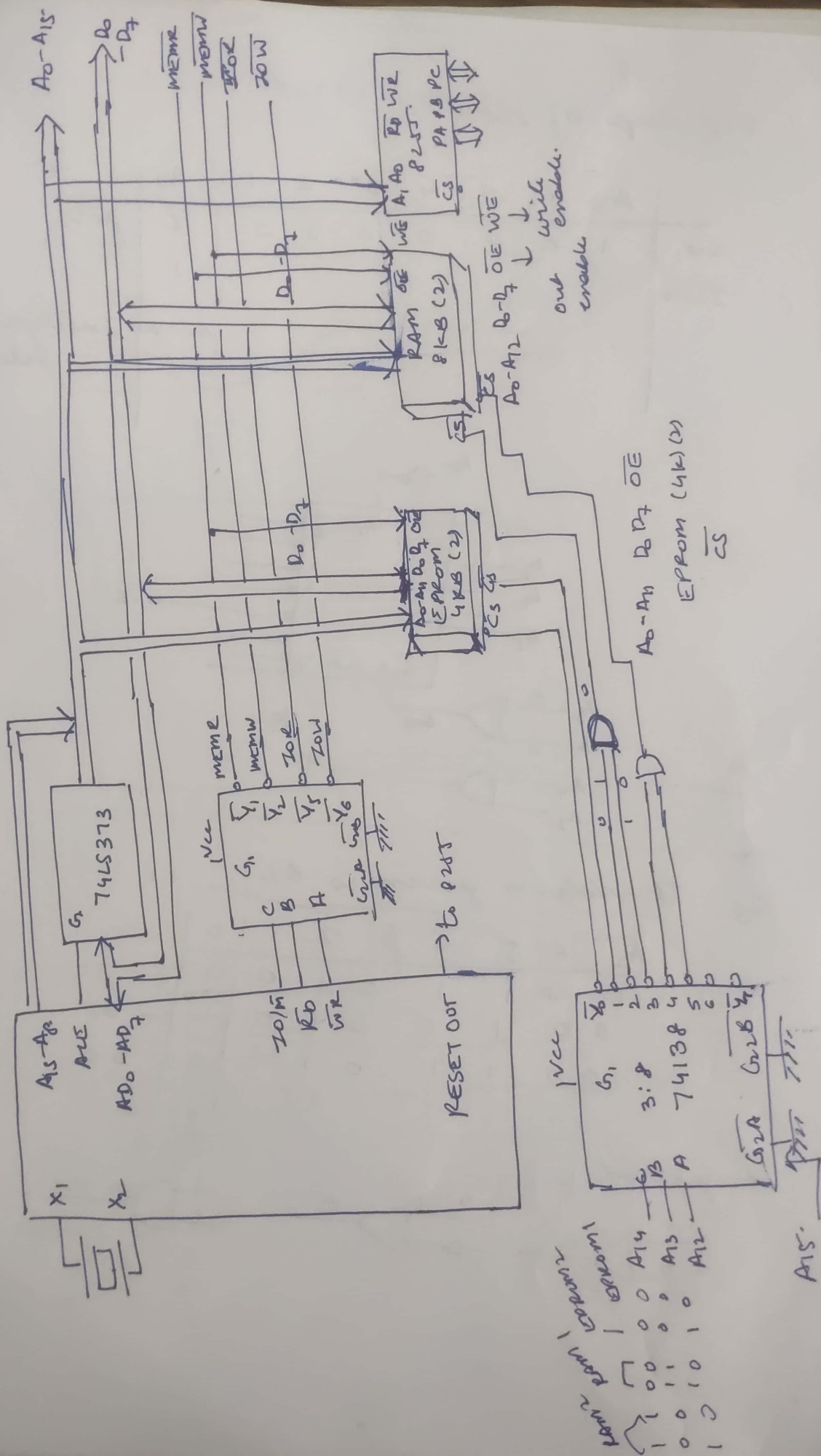
Circuit for the implementation. is as follows



I/O Map of 8259.

	A ₇	6	5	4	3	2	1	0	A ₀	
ICW ₁	1	0	0	0	0	0	0	0	0	80h
ICW ₂									1	


Internal Selection

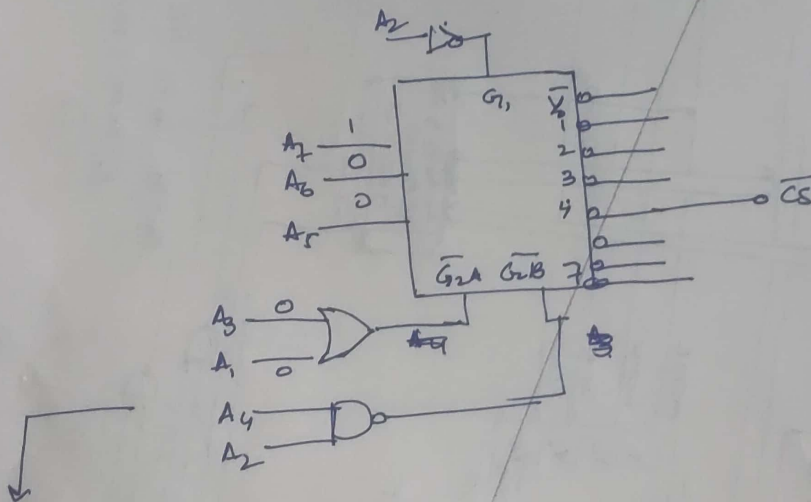

Eg If address given is 34.

A ₇	6	5	4	3	2	1	0	
0	0	1	1	0	1	0	0	- 34
0	0	1	1	0	1	0	1	- 35
0	0	1	1	0	1	1	0	- 36




In general.

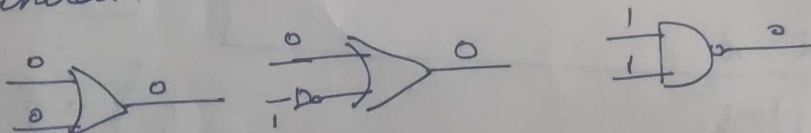

DOE 2 - BIDIRECTIONAL HANDSHAKE


I/P HIS (3)



O/P HIS (3)

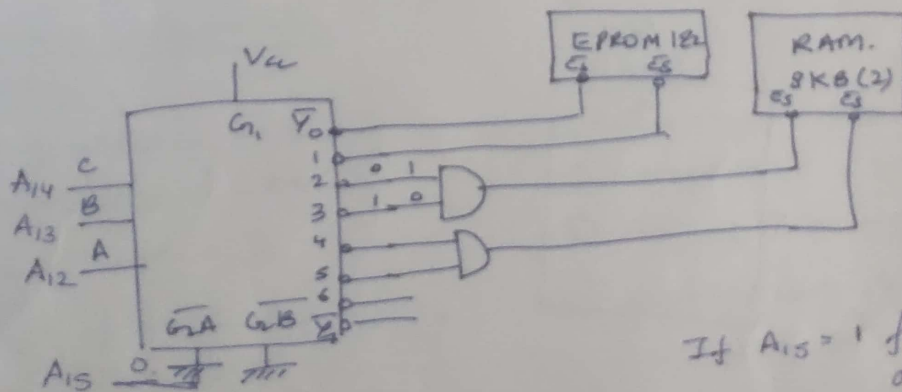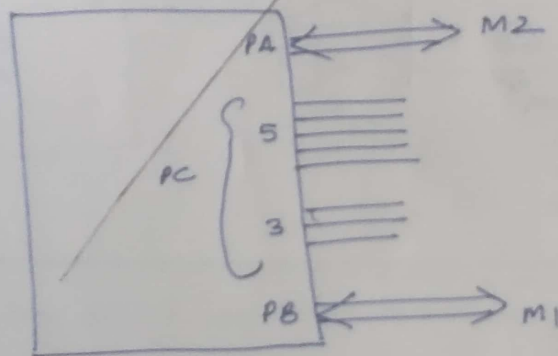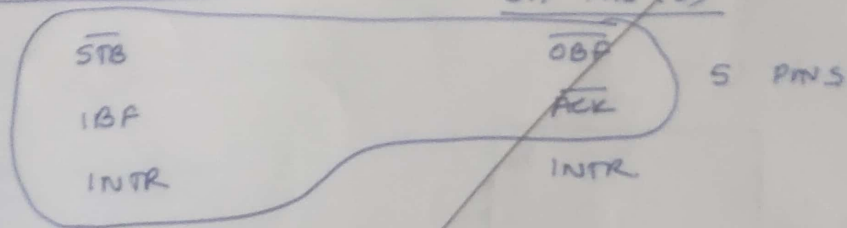


RAM 2	RAM 1	EPROM 2	EPROM 1
1	0	0	0
0	1	0	0
1	0	1	0

If $A_{15} = 1$ for any one chip then

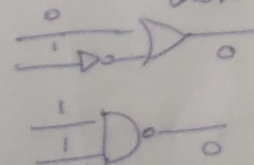


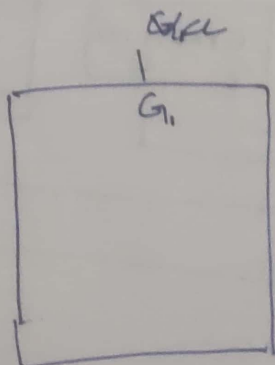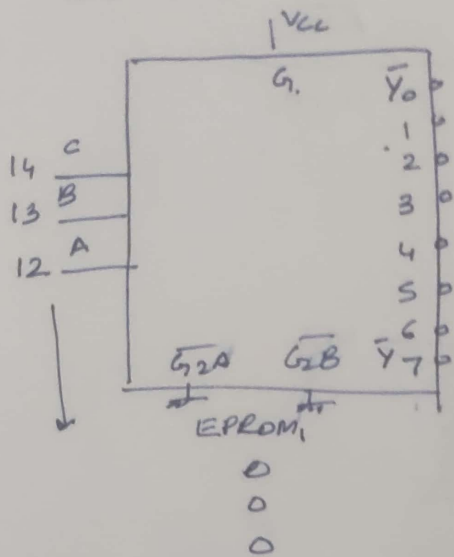

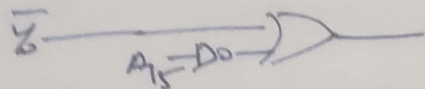in this case happens to be 0 so can be connected to ground terminal of the decoder.
 If $A_{15} = 1$ for any chip



Alternate Solution

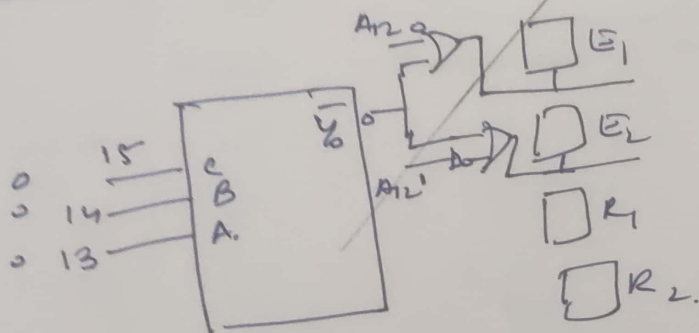

- Q. Design an 8085 system working on 3 MHz clock.
 with
 8K EPROM using 4KB chips and
 16 KB RAM using 8KB chips

Memory calculation

EPROM:

- ① Required = 8KB
- ② AVAILABLE = 4KB
- ③ No of CHIPS = 2
- ④ Size of single chip
 $= 4KB = 4 \times 1KB$
 $= 2^2 \times 2^{10}$
 $= 2^{12}$

\therefore Addr lines reqd
 $= 12$

RAM:

- ① Required = 16KB
- ② Available = 8KB chips
- ③ No. of chips reqd = 2
- ④ Size of single chip
 $= 8KB = 8 \times 1KB$
 $= 2^3 \times 2^{10}$
 $= 2^{13}$

\therefore Addr lines reqd
 $= 13$

MODES

MODE 0 - SIMPLE I/O

MODE 1 - Handshaking

MODE 2 - Bidirectional handshake mode

	M0	M1	M2
	Simple	Handshake	Bidirectional
PA	✓	✓	✓
PB	✓	✓	M1 M0
PC	✓	X → HS	X → HS

I/O Command -

7	6	5	4	3	2	1	0
IO/BSR	MODE	PA	PA	PCW	MB	PB	PC
↓	00 - M0 01 - M1 1X - M2				↓	0 - M0 1 - M1	

D7 - I/O - 1 BSR - 0

D6, D5 - Mode 0 - 00 Mode 1 - 01 Mode 2 - 1X

D4 - PA → I/O Port - 1 O/P Port - 0

D1 - PB → I - I/O 0 - O/P

D2 - Port B mode 0 - 0 Port B mode 1 - 1

PC0 - 1 - I/O 0 - O/P

PC1 - 1 - I/O 0 - O/P

Eg

1	0	0	1	0	0	1	0	- 92H
IO/BS	Mode	PA	PA	PC _n	MB	PB	PC _L	

PA - mode - 0

PB - " 0

PC mode 0 - OIP.

INPERENCE

8086 - MOV AL, 92H
OUT 86H, AL

8085 - MVI A, 92H
OUT 83H

BSR Command:- Only for Port C

CW.

0	X	X	X	PC	PC	PC	S/R
---	---	---	---	----	----	----	-----

Select a bin
000 - PC₀
...
111 - PC₇

1 - Set
0 - Reset

