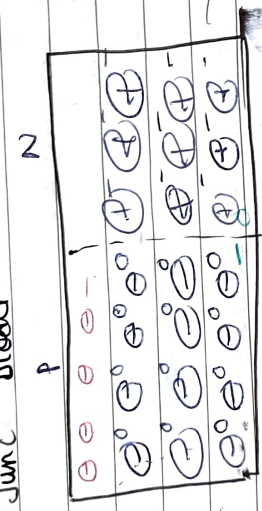


1) $e^- \rightarrow$
 \leftarrow I: (Conventional current)
 $I' \rightarrow$ Normal Current

\Rightarrow P-N Junction Diode




Bias : application of external voltage across the terminals

- ① No bias condⁿ
- ② Forward bias
- ③ Reverse :

$\leftarrow e^-$, \rightarrow holes

\therefore Diffusion current

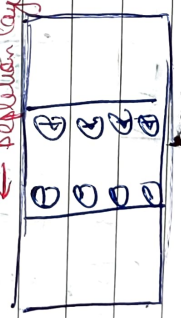due to diffusion \rightarrow unmovable ions will surface out. Depletion region has no mobile charges but only uncovered charges.



Depletion layer repels hole

\therefore Depletion layer is stagnant
 \therefore A p-n junction potential is developed

\therefore drift current due to minority charge carriers.
 At steady \rightarrow drift = diffu
 $Wd = 0$

$$V_b = \frac{kT}{e} \ln \left(\frac{N_A \cdot N_D}{n_i^2} \right), \quad V_T = \frac{kT}{e}, \quad k = 1.38066 \times 10^{-23} \text{ J/K}$$

At room temp \rightarrow Thermal voltage e^- : charge of e^-
 n_i : intrinsic

$$V_T = \frac{kT}{e} = \frac{1.38066 \times 10^{-23} \times 300}{1.6 \times 10^{-19}} = 0.0259 \text{ V}$$

width of depletion layer:

$$w_d = \sqrt{\frac{2\epsilon}{q} \left[\frac{1}{N_A} + \frac{1}{N_D} \right] V_b}$$

Page:
 Date:

$\epsilon = \epsilon_{Si} \cdot \epsilon_0$

for Si $\epsilon = 1.04 \times 10^{-12} \text{ F/cm}$

(D.E)

$\epsilon_0 = 8.85 \times 10^{-12} \text{ F/cm}$

> Forward Bias: (P-P) \therefore it will force holes \rightarrow over
 \therefore depletion layer decreases

$w_d > w_d' \therefore V_d \uparrow w_d \uparrow$

$I_d = I_{avg} - I_s$

\therefore Barrier potential is decreases

> Reverse Bias (P-N)

Dep layer \uparrow $[V_d \uparrow w_d \uparrow]$ Barrier for P is
 $(I_{avg} \approx 0)$

> Rel ϵ b/w diode current diode voltage

$I_d = I_s \left(e^{\frac{qV_d}{kT}} - 1 \right)$

diode current \downarrow I_s \downarrow $\frac{qV_d}{kT}$ \downarrow voltage across diode

$k = 1.38 \times 10^{-23} \text{ J/K} = k_B$ \downarrow Temp


$n \rightarrow$ Ideality factor $n=1$ $n=2$

for Ge when I_d low
 for Si

$\therefore I_d = I_s \left(e^{\frac{qV_d}{n k T}} - 1 \right)$

$n=1$ for both when I_d high

> V-I when $V_d = 0, I_d = 0$

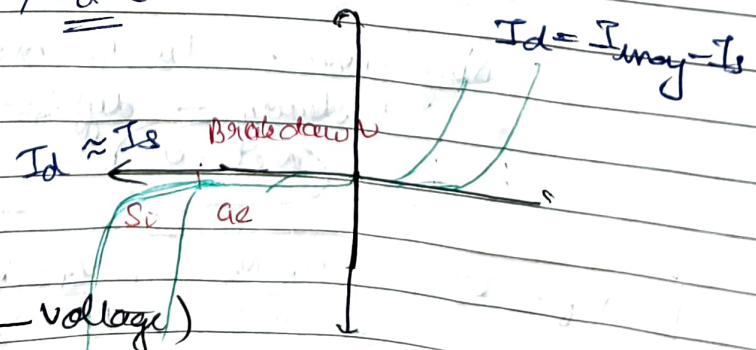


> PIV (Peak I voltage)
 Max voltage

Effects of temp In case F.B the ch. of Si diode shifts to left at 2.5 mV/deg centigrade
 $V_d \downarrow$ with temp


Page :

Date :


In R.B it doubles for every 10°C in temp $V_{DD} \uparrow$ I_{SS}

→ Rectifier alteration of A 

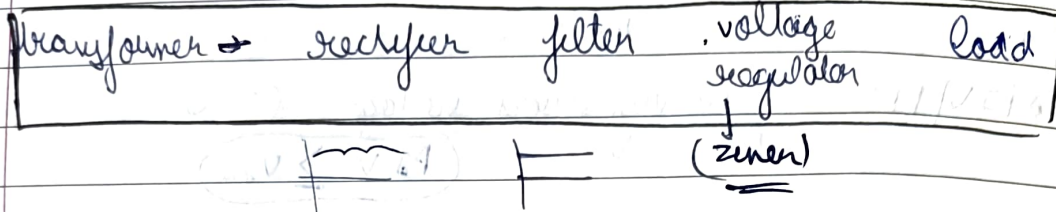IND
 $f = 50\text{Hz}$
 $f = 60\text{Hz}$



→ Half Wave:

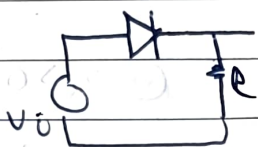

$$+V_i - V_B - I_{R_B} - I_R = 0$$

$$I = \frac{V_i - V_B}{R_B + R}$$

$$\therefore V_o = \left(\frac{V_i - V_B}{R_B + R} \right) R$$

$$\therefore V_{av} = \frac{1}{2\pi} \int_0^\pi V_m \sin \omega t \, d\omega t$$

in case of other half $V_o = 0$

$$V_{av} = \frac{V_m}{\pi} = 0.318 V_m$$

$$A_v \text{ load current} = \frac{V_{av}}{R} = \frac{0.318 V_m}{R}$$

$$I_{RMS} = \sqrt{\text{mean}(I^2)} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I^2 \, d\omega t} = \frac{I_m}{2}$$

$$V_{RMS} = \frac{V_m}{2}$$

→ Form factor. (Ratio of RMS load voltage, average load vol)
 $\frac{V_{RMS}}{V_{av}} = \frac{V_m/2}{V_m/\pi} = \frac{\pi}{2} = \frac{I_{RMS}}{I_{dc}}$

$$F.F \geq 1$$

→ Ripple factor: The ripple factor measures the percent of ac comp in rectified out
 $(\gamma = 0.9)$

$$\gamma = \frac{\text{rms value of ac comp of o/p}}{\text{av. value of o/p}}$$

$$I = I_{ac} + I_{dc}$$

$$= [I_{RMS}^2 + I_{dc}^2 - 2I_{ac}I_{dc}]$$

$$= \sqrt{I_{RMS}^2 - I_{dc}^2}$$

$$I_{ac} \text{ RMS} = \left[\frac{1}{2\pi} \int_0^{2\pi} (I - I_{dc})^2 \, d\omega t \right]^{1/2}$$

$$F-F=1.57$$

$$=121\%$$

Page :

Date :

→ efficiency : $\frac{\text{D.C power available}}{\text{input ac power}} = \frac{P_{\text{load}}}{P_{\text{in}}}$

$$= \frac{I_{dc}^2 R}{I_{Rm}^2 R} \times 100\% = \frac{(I_{Rm}/\pi)^2}{(I_{Rm}/2)^2}$$


$$= 40.56\%$$

→ PIV/PRV: maximum reverse voltage ($I=0$)

$$PIV = V_m$$

$$PIV \geq V_m$$

→ Full Wave Rectifier (Bridge)

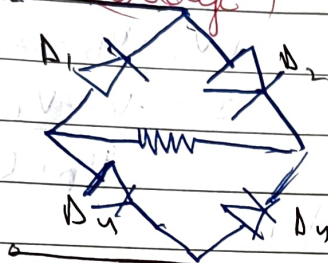


① $V_i > 0$, D_1, D_3 : FB

$$V_o = V_i / V_i - 2V_B / V_i - 2V_B - 2I_{B1}$$


② $V_i < 0$, D_2, D_4 : FB

$$V_o : \text{Same}$$

if capacitor filtered

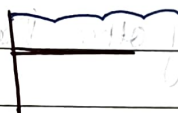

Center Tapped

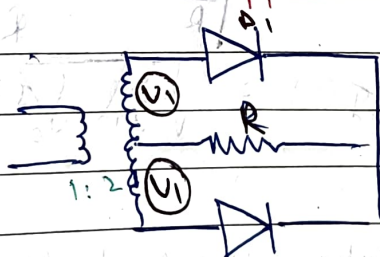

$$\frac{N_p}{N_s} = \frac{V_p}{V_s}$$

$$1/2 = \frac{V_p}{V_s}$$

$$\therefore V_s = 2V_i$$

one FB, other RB

→ Avg. load current/voltage (AC)

$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d\omega t = \frac{2V_m}{\pi}$$

$$I_{av} = \frac{2I_{Rm}}{\pi}$$

→ RMS

$$= \sqrt{\frac{1}{\pi} \int_0^{\pi} I^2 d\omega t} = \frac{I_{Rm}}{\sqrt{2}}$$

$$V_{RMS} = \frac{V_m}{\sqrt{2}}$$

→ F.F:

$$\frac{V_m/\sqrt{2}}{2V_m/\pi} = 1.11$$

$$\rightarrow R_o F = 48.1\%$$

$$\text{efficiency} = \frac{(2\pi)^2}{\pi^2} = \frac{8}{\pi^2} = 81.18\%$$

PIV

Bridge: in R.B. for any diode

$$= V_m$$

first find V_o
then KVL

Center: $V_o = V_m$

$$= 2V_m$$


$$PIV \geq 2V_m$$

Page:

Date:

Clippers: Network that uses diodes for ~~this purpose~~ to clip a portion of input signal without distorting the remaining part
Can be used to remove clippers

depends on which polarities clipped

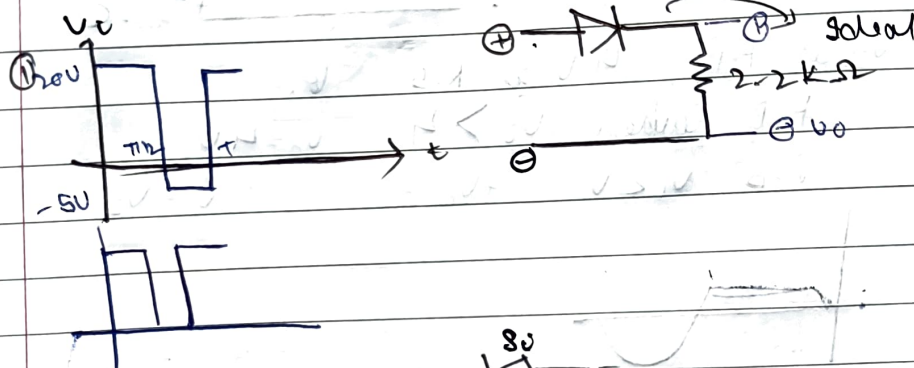


$$V_I + 0.7V_o - V_o = 0 \therefore V_o = V_I + 0.7V$$

$$V_I + V_o - 0.7V = 0 \therefore V_o = 0.7 - V_I$$

$V_o > V_B$




already consider $V_o = -ve$

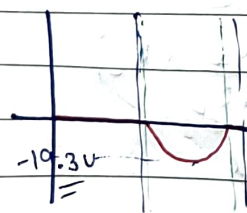

first find state of diode

$$V_I + 5 - 0.7V = V_o = 14.3V$$



$$V_o = 0 \text{ / No current}$$

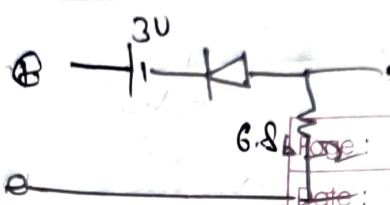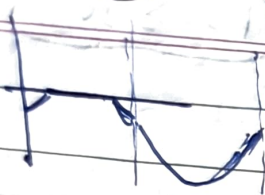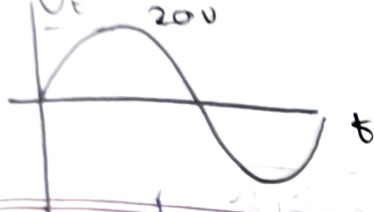



Page: _____

Date: _____

→ Parallel

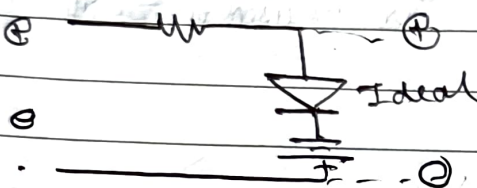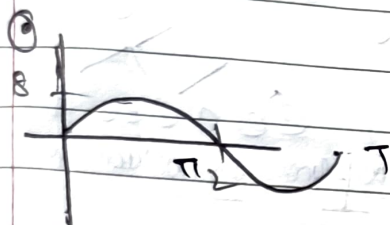

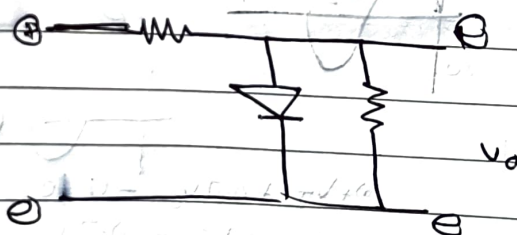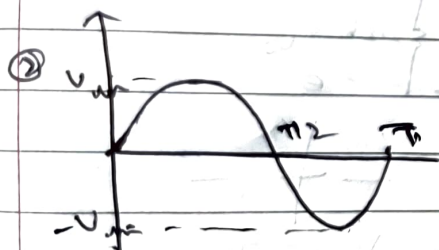V_I is F-B, $4V$ is R-B V_I
 \therefore F-B when $V_i > 4$ $V_o = 4V$
 R-B $V_i < 4$ $+V_o - V_i = 0 \therefore V_o = V_i$



When (R-B) $= V_I - I(R+R_L)$



$$\therefore V_o = \frac{V_I \times R_L}{R+R_L}$$

when R small

⇒ **Clampers**: Network constructed of diode, resistor and capacitor that shifts the waveform to a different dc level without changing the appearance of applied


$$Z_{ca} = (RC)$$

$$Z \gg T/2$$

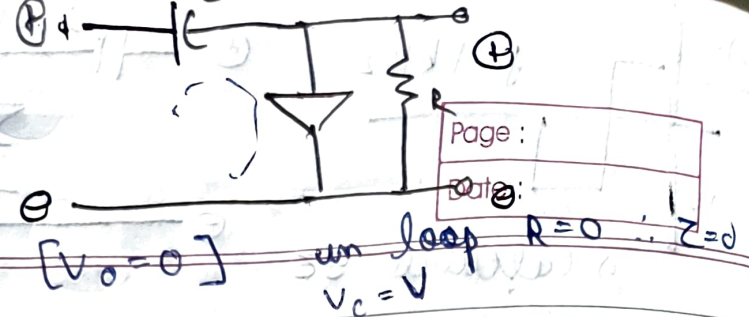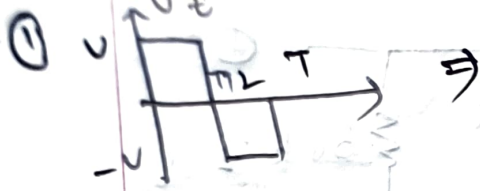


$0 = T/2 \rightarrow \text{F.B. } [V_o = 0] \quad \text{an loop } R=0 \therefore Z=0$
 $V_c = V$

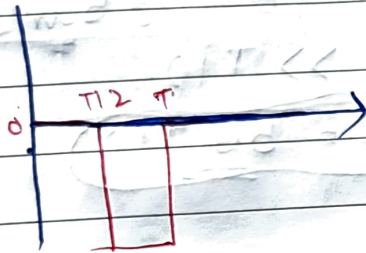$T/2 \rightarrow T \rightarrow \text{R.B. } +V_i + V_o + V = 0 \therefore V_o = (-V_o - V)$
 $= -2V$




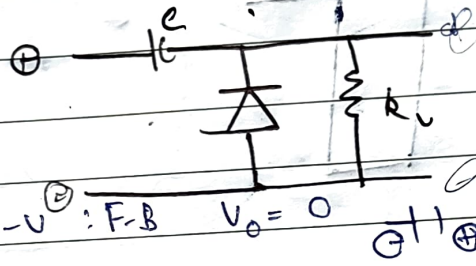
- ① RMS remain same
 - ② Peak value changes
- \Rightarrow Negative Clamper



$0 \leq T/2 \quad V_i = V \therefore \text{F.B. } V_o = 0 \quad V_c = V_i = V$

$T/2 \rightarrow T \quad V_o = V_o = V_i + V_c = 2V$

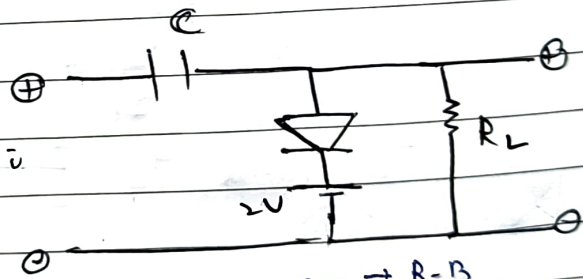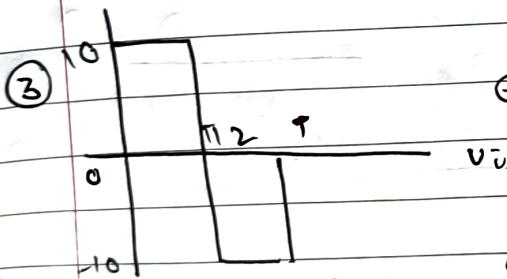$d \cdot t = \infty \rightarrow 0 \therefore$ won't discharge




$V_c \rightarrow \text{F.B.}$

$0 \rightarrow T/2 \quad : V_c = 10V \therefore \text{F.B. since } V_i > 2$
 $V_o = 2V, \quad V_c = (V - 2) = 8V$

$T/2 \rightarrow T \quad V_c = -10V$

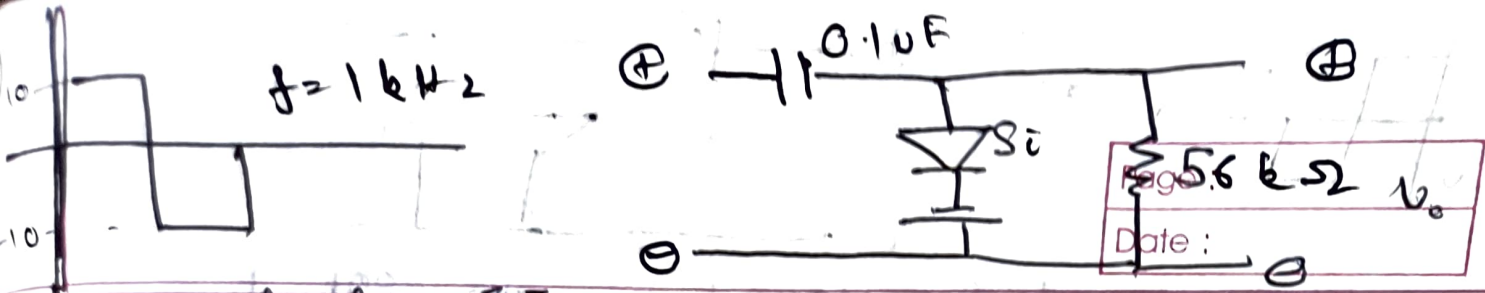$V_c + V_o + V_c = 0 \therefore V_o = -2V_c - V_c$
 $= -10V - 8V$
 $= -18V$





- 1) Calculate SZ
- 2) Compare SZ to half time period
- 3) Sketch V_o .

$$\text{SZ} = 2.8 \text{ mks}$$

$$T_{12} = 10^{-4} \text{ s} = 0.5 \text{ mks}$$

$$\therefore \text{SZ} \gg T_{12}$$

$$\text{SZ} = 56 T_{12}$$

