

FCEC003_CSE1_Class Test 2

chiragsaini.ug21@nsut.ac.in [Switch account](#)


 Draft saved

Your email will be recorded when you submit this form

FCEC003_CSE1_Class Test 2 Questions

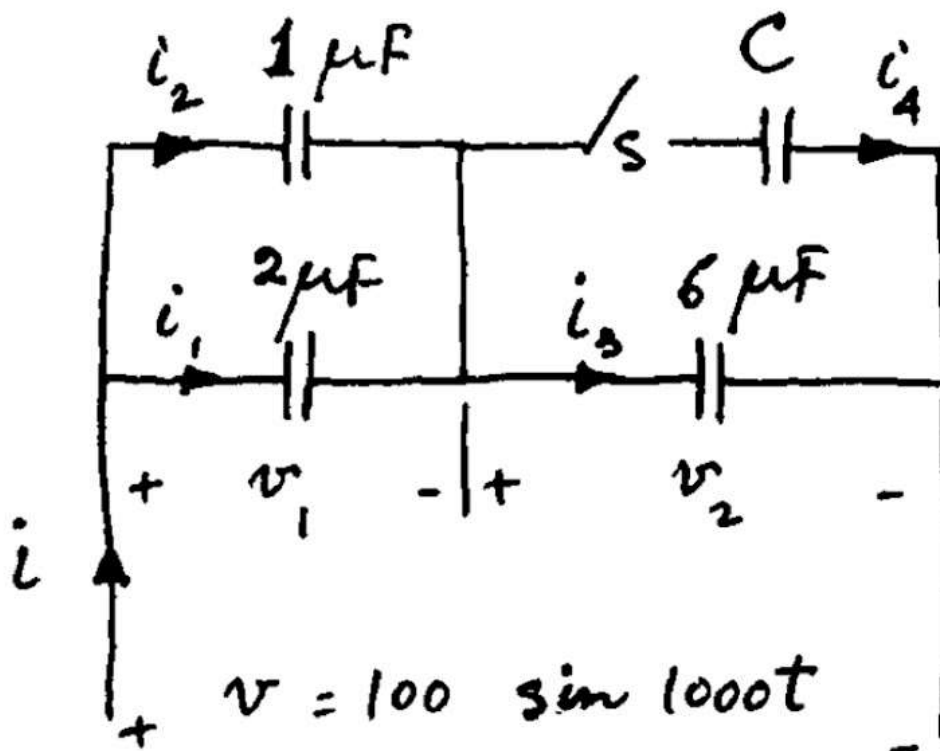1. Attempt all questions.
2. NO negative marking.
3. Assume suitable data wherever applicable.
4. NO Quiz response shall be recorded after the stipulated time.
5. Do not refresh webpage and don't use back button during test.
6. Do not open any new tab during test.
7. Only ONE response per student. Once submitted a student can't attend the test again.
8. Click "Back" to go to previous section.

For the circuit shown in fig., determine v_1 and v_2 (in V) when switch, S is open. 2 points




- ☐ $v_1 = 33.333 \sin 1000t, v_2 = 66.667 \sin 1000t$
- ☒ $v_1 = 66.667 \sin 1000t, v_2 = 33.333 \sin 1000t$
- ☐ $v_1 = v_2 = 50 \sin 500t$
- ☐ $v_1 = v_2 = 50 \sin 1000t$

[Clear selection](#)

For the circuit shown below., calculate the current (I) supplied by the voltage source. ($j = \sqrt{-1}$)

2 points

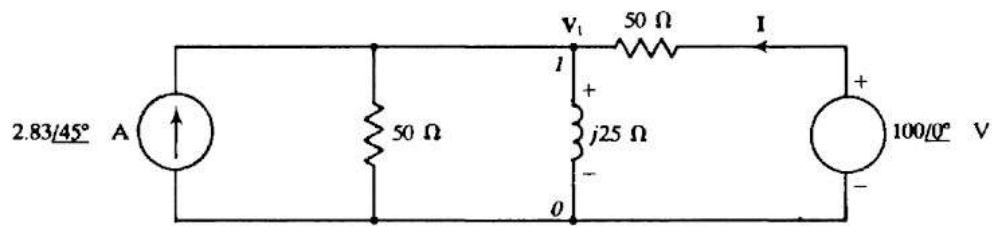


- ☐ 15 - j15, A
- ☐ 3.5 - j3.5, A
- ☒ 1.5 - j1.5, A
- ☐ 35 - j35, A

Clear selection

A $30\text{-}\mu\text{F}$ capacitor is charged by a voltage source having sawtooth waveform shown in fig. Determine the charging current.

2 points

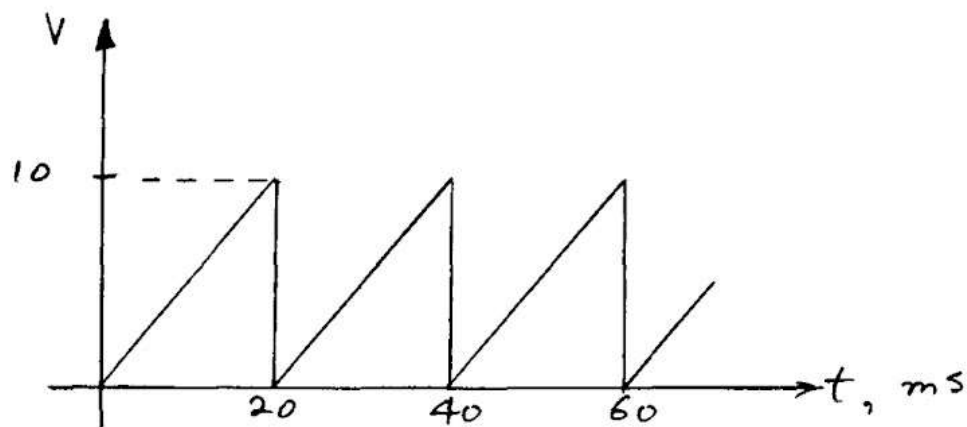


- ☒ 15 mA
- ☐ 10 A
- ☐ 15 A
- ☐ 20 mA

Clear selection



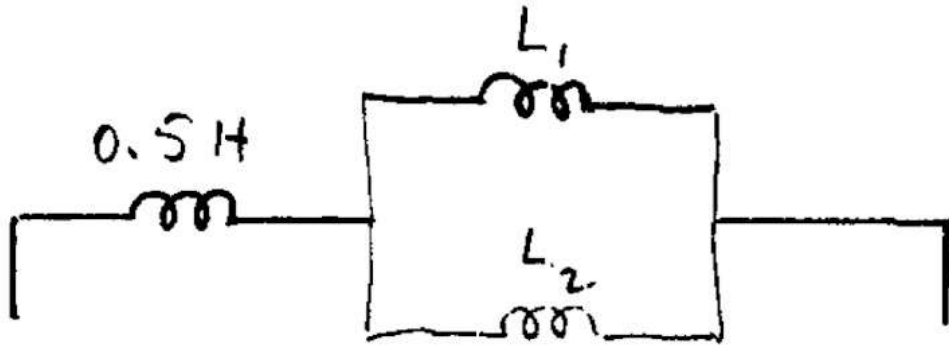Given $L_1 = 2L_2$, find L_1 and L_2 , respectively, if equivalent inductance is 0.7H . 1 point



- ☐ None of the above
- ☐ 2H and 1H
- ☐ 0.3H and 0.6H
- ☒ 0.6H and 0.3H

Clear selection

A current $i = 10 \cos 377t$, A is switched through a $10\text{-}\mu\text{F}$ capacitor at $t = 0$. Determine the rms voltage across the capacitor and the charge associated with it. 1 point

- ☐ 377V and $377 \sin 10t$, C
- ☐ 187.6V and $26.525 \sin 377t$, C
- ☐ $265.25 \sin 377t$ and $26.525 \sin 377t$, mC
- ☒ 187.6V and $26.525 \sin 377t$, mC

Clear selection




A 4ohm resistor in series with a 7.96mH inductor is connected across a 110-V, 60-Hz supply. Determine: (a) impedance, Z (b) supply current, I (c) voltage across resistor, V_r and (d) voltage across inductor, V_L . 2 points

- ☐ (a) $\text{mag}(Z) = 5$, $\text{ang}(z) = 36.87^\circ$; (b) $\text{mag}(I) = 22$, $\text{ang}(I) = -36.87^\circ$; (c) $\text{mag}(V_r) = 88$, $\text{ang}(V_r) = 0^\circ$; (d) $\text{mag}(V_L) = 66$, $\text{ang}(V_L) = 53.13^\circ$
- ☐ (a) $\text{mag}(Z) = 3$, $\text{ang}(z) = -36.87^\circ$; (b) $\text{mag}(I) = 22$, $\text{ang}(I) = -36.87^\circ$; (c) $\text{mag}(V_r) = 88$, $\text{ang}(V_r) = 0^\circ$; (d) $\text{mag}(V_L) = 66$, $\text{ang}(V_L) = 53.13^\circ$
- ☐ (a) $\text{mag}(Z) = 5$, $\text{ang}(z) = -36.87^\circ$; (b) $\text{mag}(I) = 22$, $\text{ang}(I) = -36.87^\circ$; (c) $\text{mag}(V_r) = 88$, $\text{ang}(V_r) = -36.87^\circ$; (d) $\text{mag}(V_L) = 66$, $\text{ang}(V_L) = 53.13^\circ$
- ☒ (a) $\text{mag}(Z) = 5$, $\text{ang}(z) = 36.87^\circ$; (b) $\text{mag}(I) = 22$, $\text{ang}(I) = -36.87^\circ$; (c) $\text{mag}(V_r) = 88$, $\text{ang}(V_r) = -36.87^\circ$; (d) $\text{mag}(V_L) = 66$, $\text{ang}(V_L) = 53.13^\circ$

Clear selection



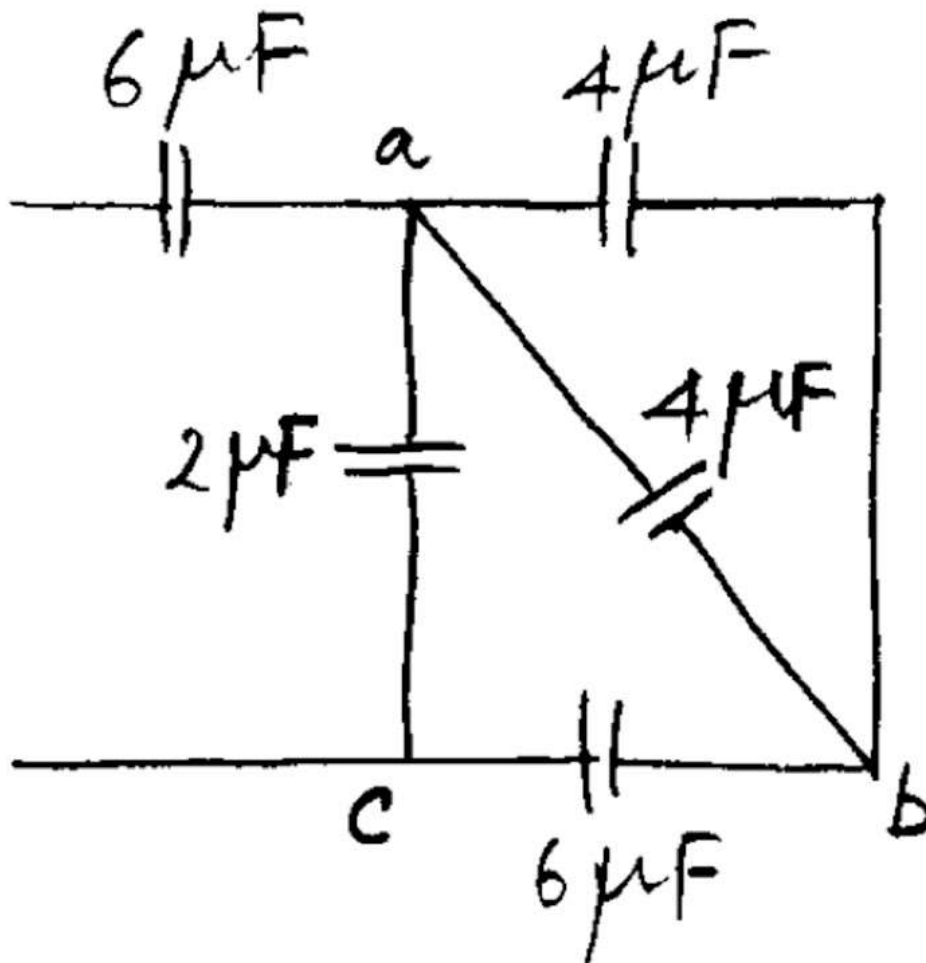Find the equivalent Capacitance (in micro Farad) of the combination shown in fig. 1 point




- ☐ 5.43
- ☐ 6
- ☒ 2.85
- ☐ 10

Clear selection



An inductive load takes 480W of power at 0.8 power factor, while operating at 120V and 60-Hz. It is desired to make power factor of input current (w.r.t. input voltage) unity by connecting a capacitor in parallel with the inductor. What is the value of the capacitance.

1 point

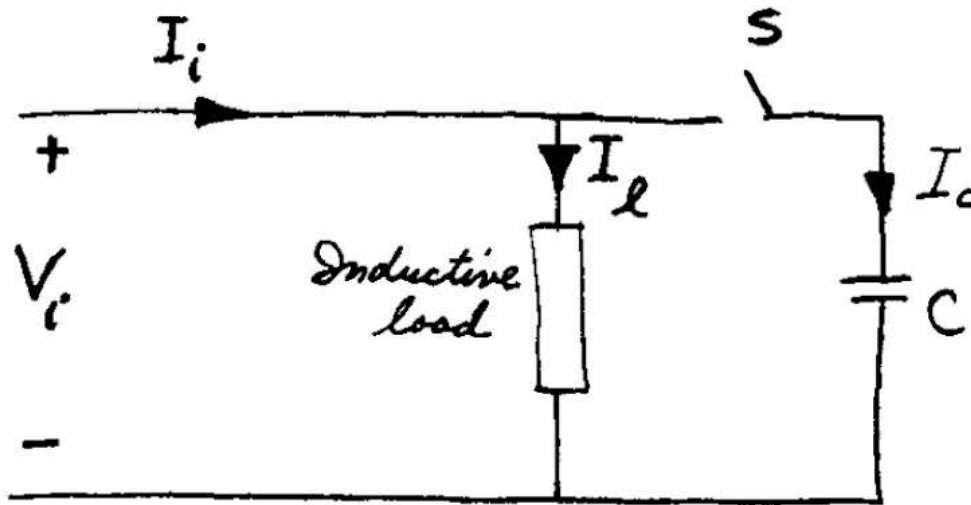

- ☒ 66.3micro-Farad
- ☐ 33.2micro-Farad
- ☐ 11micro-Farad
- ☐ None of the above

Clear selection

The bandwidth of a series (RLC) resonant circuit is 500 Hz. Resonant frequency is 6kHz, and if $R = 10 \Omega$, calculate the inductance (L) and capacitance (C) of the circuit.

1 point

- ☐ L = 3.18H and C = 0.22micro-Farad
- ☐ L = 6.37H and C = 0.22micro-Farad
- ☒ L = 3.18mH and C = 0.22micro-Farad
- ☐ L = 6.37mH and C = 0.22micro-Farad

Clear selection



Which of the following is false at resonance?

1 point

- ☒ Peak energies stored by the inductor and the capacitor are equal.
- ☐ Energy shuttles to and fro between inductor and capacitor.
- ☐ No energy is taken from the source by the inductor and capacitor.
- ☐ None of the above

Clear selection

For a resistor in series with a inductor connected across a AC supply, which of the following is true ?

1 point

- ☐ Total Supply Average Power = Average Power dissipated in Inductor
- ☐ Total Supply Average Power = Power in Inductor + Power in resistor
- ☒ Total Supply Average Power = Average Power dissipated in resistor
- ☐ Total Supply Average Power = Power in Resistor - Power in inductor

Clear selection

Page 2 of 2

Back

Submit

Clear form

Never submit passwords through Google Forms.

This form was created inside of Netaji Subhas University of Technology. [Report Abuse](#)

Google Forms

