

* Semiconductors: Their conductivity lies between conductors & insulators.
 \Rightarrow Si, Ge imp.

* Energy Band: Energy given to an e^- for reaching the conduction band.
 $[E_g]$ $E_g)_{Si} \approx 0.7 \text{ eV}$ $E_g)_{Ge} \approx 0.3 \text{ eV}$ {at Room temperature}
 also as $[T \uparrow \quad E_g \downarrow \quad \sigma \uparrow \quad R \downarrow]$

* Currents in a semiconductor
 1. Hole current: \swarrow
 2. Electron current: \searrow
 Net: Hole current + Electron current
 e^- & hole move in opposite dirn but current flow in same direction.

* Maths of General S.C.

$$i_{sc} = i_n + i_p \quad \& \quad i = JA = nAeV_d = \sigma EA$$

$$\sigma = ne\mu = ne \frac{V_d}{E} = \sigma$$

$$\sigma_{sc} = e[n\mu_n + p\mu_p] \quad \text{imp.}$$

μ = mobility J : Current density
 σ : conductivity
 E : EF
 V_d : Drift current
 e : $1.61 \times 10^{-19} \text{ C}$

also for neutrality: $\underbrace{n + N_p}_{\text{negative charges}} = \underbrace{N_n + p}_{\text{+ve charges}}$

& by mass action law

$np = n_i^2$
 $\swarrow \quad \downarrow \quad \searrow$
 electron change density \quad hole change density \quad intrinsic change density

Types of Semiconductors:

Intrinsic

$$p + N_n = n + N_p$$

$$N_n = 0 = N_p \quad \checkmark$$

$$p = n \quad \checkmark$$

$$\boxed{n = n_i = p}$$

$$\sigma = n_i e [\mu_n + \mu_p]$$

Extrinsic

Grp 13

p-type [B, Al, Ga, In]

$$p \gg n$$

$$N_n = 0$$

$$N_p \approx p$$

$$\boxed{n = \frac{n_i^2}{N_p}}$$

$$\sigma \approx N_p \mu_p e$$

Grp 15

[P, As, Sb]

n-type

$$p \ll n$$


$$N_p = 0$$

$$N_n \approx n$$


$$\boxed{p = \frac{n_i^2}{N_n}}$$

$$\sigma \approx N_n \mu_n e$$

Semiconductor Diode:

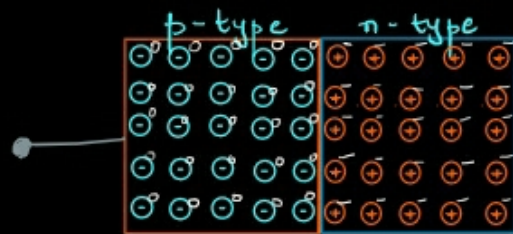


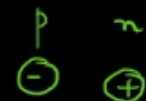diffusion begins from n region to p of the e-s or i_d [p \rightarrow n]



Bowen Potential

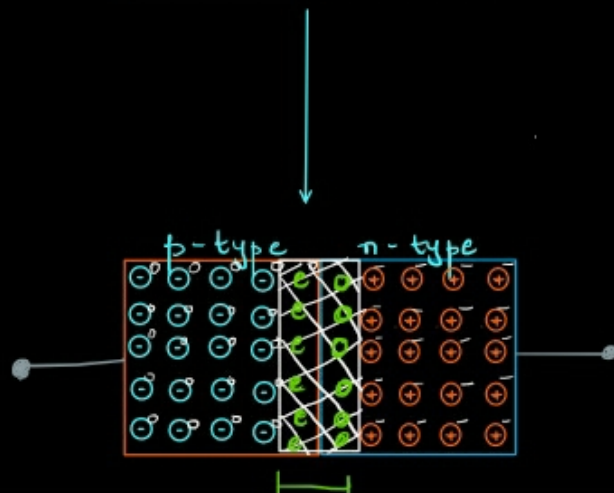ϕ \rightarrow Built in potential
 $\mathcal{E} \leftarrow$



$$\text{Here: } J_{\text{net}} = 0 = \underbrace{i_{\text{diff}}}_{p \rightarrow n} - \underbrace{i_{\text{drift}}}_{n \rightarrow p}$$

$$[i_{\text{drift}} = i_{\text{diff}}]$$

for no biasing or Potential

and for no bias:

$$V_B = V_T \ln \left[\frac{N_p \cdot N_n}{n_i^2} \right] \left(\frac{k}{e} \right) T$$

where $k \Rightarrow$ boltzmann constant

$$e \Rightarrow 1.61 \times 10^{-19} \text{ C}$$

$$k/e = 1/11600$$

$[V_B]$

$$V_B = \frac{T}{11600} \ln \left\{ \frac{N_p \cdot N_n}{n_i^2} \right\} *$$

for $T = 300 \text{ K}$ or RT

$$V_T = 0.026 \text{ V}$$

$$V_B = 0.026 \ln \left[\frac{N_p \cdot N_n}{n_i^2} \right]$$

$$V_T = T/11600 *$$

$[W_D]$


width

$$W_D = \sqrt{\frac{2\epsilon}{e} \cdot \left[\frac{1}{N_p} + \frac{1}{N_n} \right] V_T \cdot \ln \left(\frac{N_p N_n}{n_i^2} \right)}$$

$$\left\{ \epsilon : \text{permittivity} = \epsilon_r \epsilon_0 \right\}$$

$$[V_T : T/11600]$$

Forward Bias

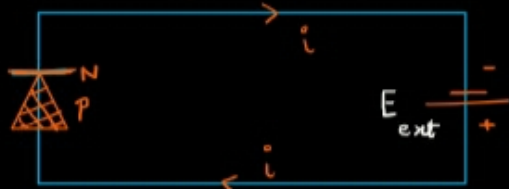


$$i = i_{diff} - i_{drift}$$

$$\text{here } \{ V_B' = V_B - E_{ext} \}$$

\rightarrow here Barrier potential \downarrow
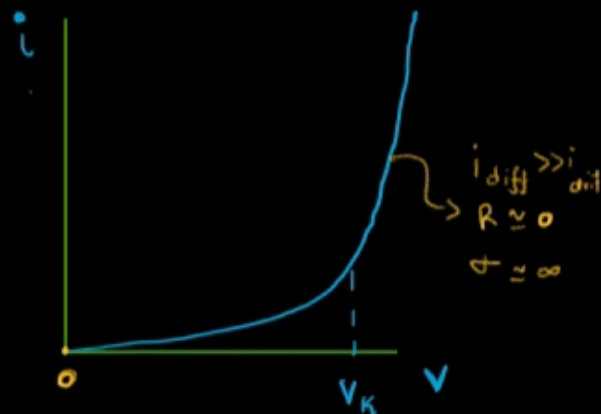
$$i_{diff} \gg i_{drift} \rightarrow i = i_{diff}$$



Reverse Bias

V_Z

Reverse Bias




$$i = -i_{diff} + i_{drift}$$

$$\text{here } \{V_B' = V_B + E_{ext}\}$$

→ have barrier potential ↓

$$\rightarrow i = i_{diff}$$

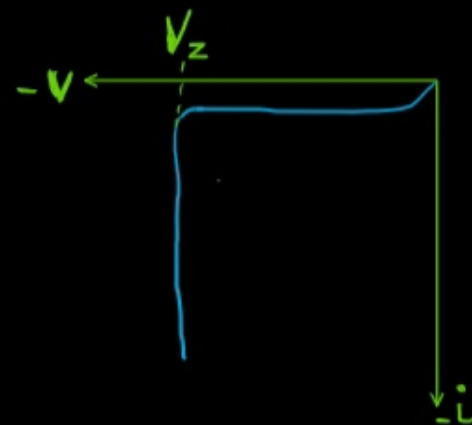

* Diode-Voltage Relationship :

[V_d = Voltage across diodes]

$$\frac{I_{diode}}{I_{saturation}} = e^{\frac{k V_d}{T}} - 1$$

$$\frac{I_d}{I_s} = e^{\frac{V_d}{V_t} \cdot \frac{1}{n}} - 1$$

Imp.

$$k = \frac{e}{k_B n} = \frac{1.6 \times 10^{-19}}{11600 n}$$

Boltzmann constant

$n = 1$ for Si (for high I_d)

$n = 2$ for Si (for low I_d)

$$\frac{k}{T} = \left(\frac{e}{k_B T} \right) \frac{1}{n} = \frac{1}{n \cdot V_T}$$

* Effect of Temperature on V-I characteristics




FB :

as temperature inc the V_0 decrease by $0.25 \text{ V} / 100^\circ \text{C}$

$$V_{T'} = V_T - (25) \Delta T$$

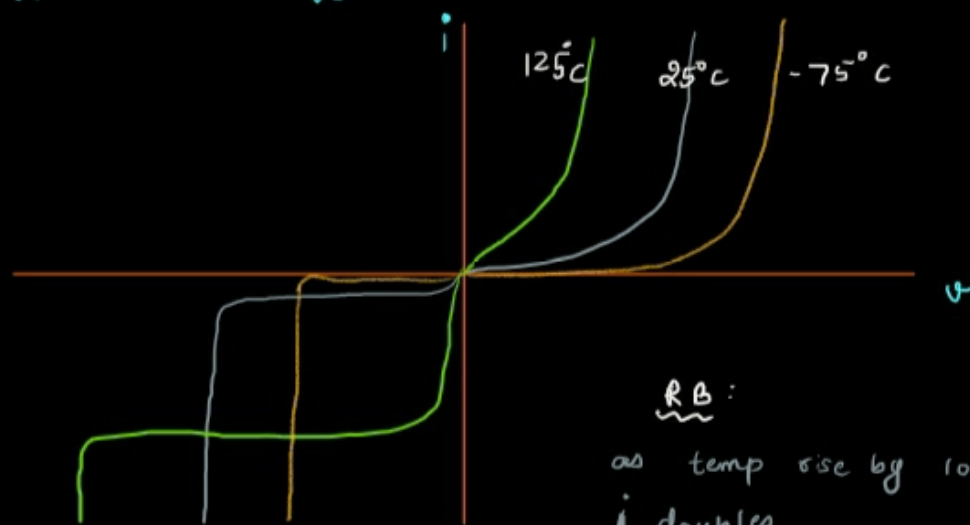* Effect of Temperature on V-I characteristics



RB:
as temp rise by $10^\circ\text{C} \rightarrow$ the i_{Sat} doubles

$$i_{T'} = i_T \cdot (2)^{\frac{T' - T}{10}}$$

FB:

as temperature inc the V_b decrease by $0.25\text{V}/100^\circ\text{C}$

$$V_{T'} = V_T - \left(\frac{25}{10^4}\right) \Delta T$$

$$[V_b \propto \Delta T]$$

* Diode Equivalent ckt:

Ideal: $\{R_d = 0 = V_d\}$

i) Piece-wise Defined ckt:



ii) for constant Voltage/Simplified eqn ckt

$$R_d = 0 \quad V_d \neq 0$$



* Load Line Analysis:



$$V - V_d = (R_L + R_D) i$$


$$\text{or } \boxed{\frac{V - V_d}{R_L + R_D} = i}$$

Diode line

$$V_d = V - i R_L$$


Q point or operating point

* Load Line Analysis :

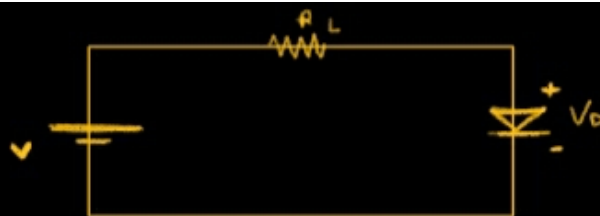

$$V - V_D = (R_L + R_D) i$$
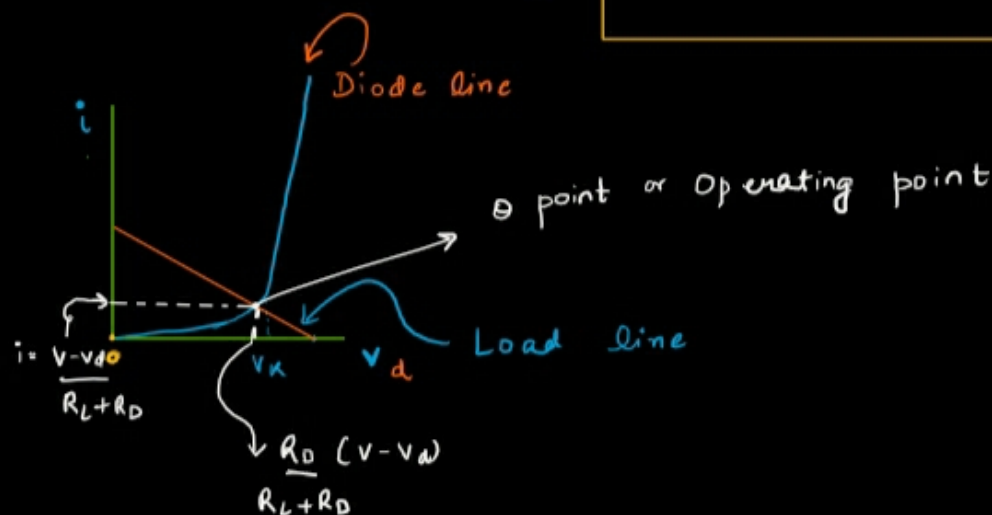
$$\text{or } \boxed{\frac{V - V_D}{R_L + R_D} = i}$$



$$V_D = V - i R_L$$


$$-\frac{V_D}{R_L} + \frac{V}{R_L} = i$$

* Resistances

i) DC Resistance

for DC voltage connected this graph don't varies.

$$R = \frac{1}{\text{slope}} = \frac{i}{V} \Big|_{\text{point}}$$

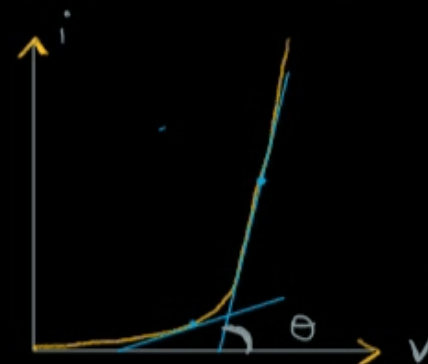


ii) AC Resistance

$$I_D = I_S (e^{V_D / n V_T} - 1)$$

$$\frac{dI_D}{dV_D} = I_S \cdot \frac{1}{n V_T} \cdot e^{V_D / n V_T}$$

$$R = \frac{dV_D}{dI_D}$$

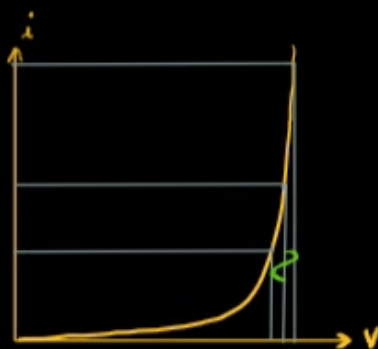

$$R = \frac{n V_T}{I_S e^{V_D / n V_T}} = \frac{n V_T}{I_D + I_S}$$

$$I_S \ll I_D \longrightarrow R = \frac{n V_T}{I} = \frac{n \cdot T}{11600 I}$$

$$R = 52 \text{ m}\Omega$$

$$R = 26 \text{ m}\Omega$$

$$T = 300 \text{ K}$$


$$R = \frac{n V_T}{I_S e^{V_D / n V_T}} = \frac{n V_T}{I_D + I_S} \quad I_S \ll I_D \longrightarrow R = \frac{n V_T}{I} = \frac{n \cdot T}{11600 I}$$

$$\boxed{R = \frac{52 \text{ mV}}{I}} \quad \text{or} \quad \boxed{R = \frac{26 \text{ mV}}{I}} \quad \leftarrow \begin{array}{l} T = 300 \text{ K} \\ n = 1 \end{array}$$

for $\boxed{n=2}$ low I value.


high values of I for Si or Ge (acc)

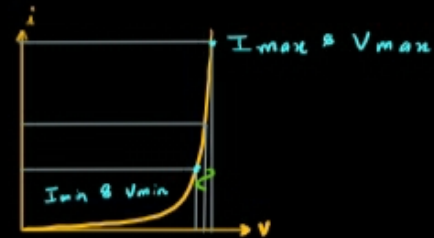iii) Avg. AC Resistance: avg AC $R = \frac{V_{\max} - V_{\min}}{I_{\max} - I_{\min}}$






Questions:


Q1: find I .

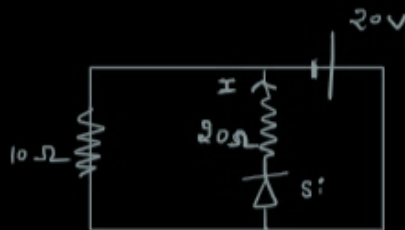


Q2: find V_o & I_D . $\{R_D \approx 0\}$

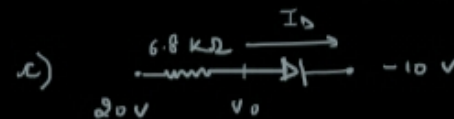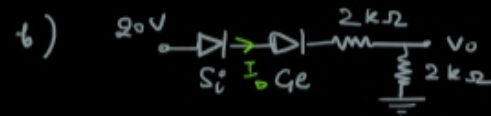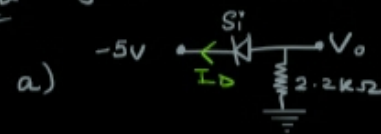




Q3

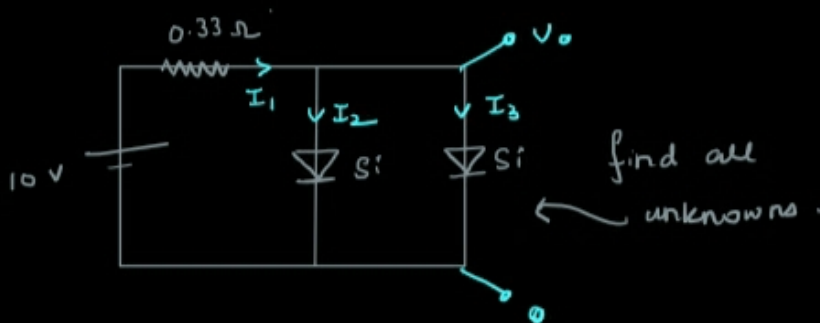



Q5

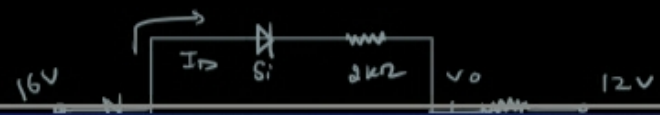

Q4 Determine V_o & I_D .

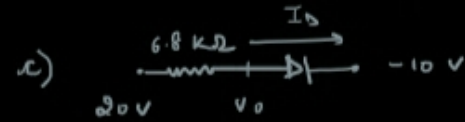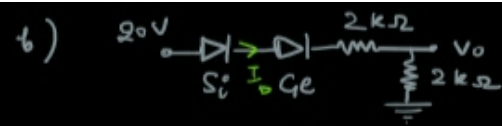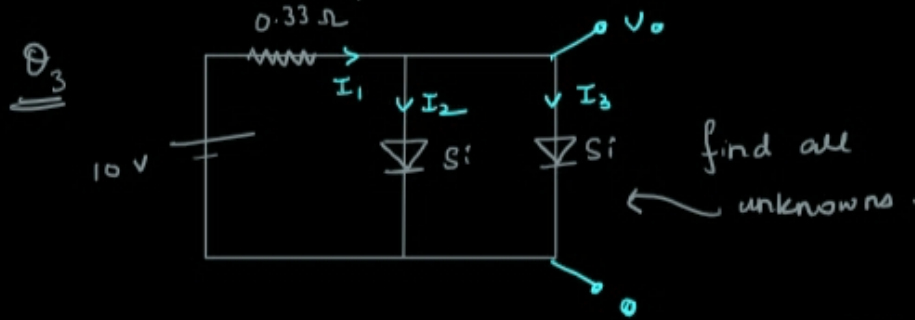

Q4 Determine V_0 & I_0 .

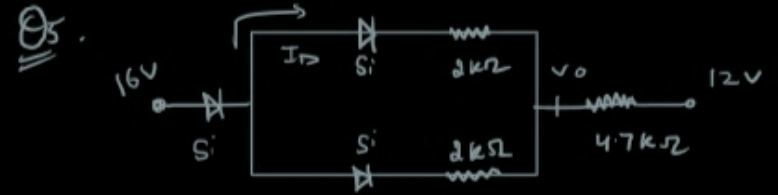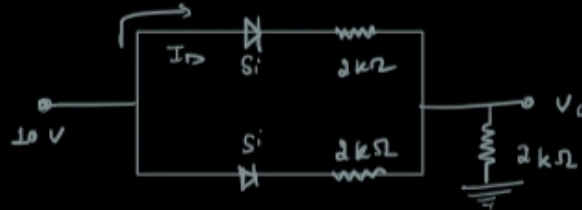

Rectifiers : Terms used :

a) avg value : $\frac{\int_0^{2\pi} f(\omega t) \cdot d(\omega t)}{2\pi}$
DC value :

b) RMS value : $\sqrt{\frac{\int_0^{2\pi} [f(\omega t)]^2 d\omega t}{2\pi}}$

c) Form-factor or FF : $\frac{V_{rms}}{V_{dc}}$


d) Ripple factor (γ) :
 (AC comp. in output) $\gamma = \sqrt{F.F.^2 - 1}$ or $\gamma = \frac{\text{RMS value of ac component}}{\text{avg. value of output.}}$

e) η (efficiency) = $\frac{P_{avg}}{P_{rms}} \cdot 100 = \frac{100}{(FF)^2}$


i) Half wave Rectifier :



fb : $[V_i - V_d = V_0]$

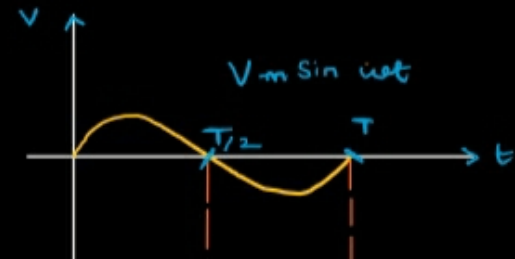

i) Half wave Rectifier:

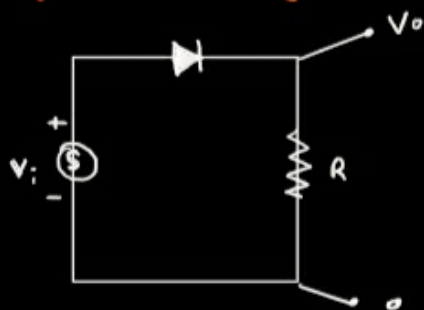


fb:

$$[v_i - v_d = v_o]$$


Rb:

$$i = 0$$


$$\{v_o = 0\}$$

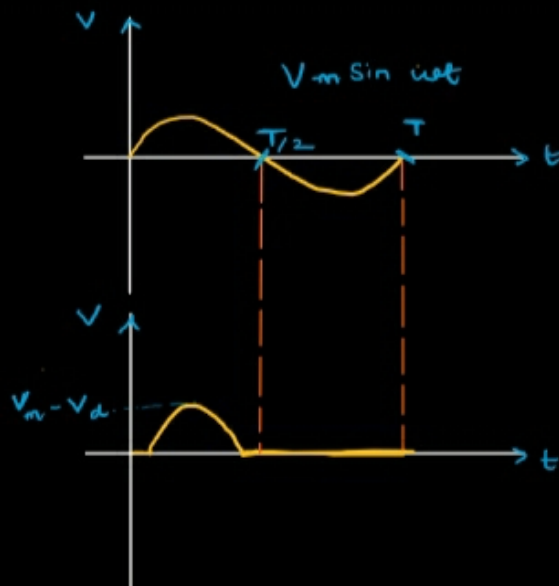

ii) Full-wave Rectifier:

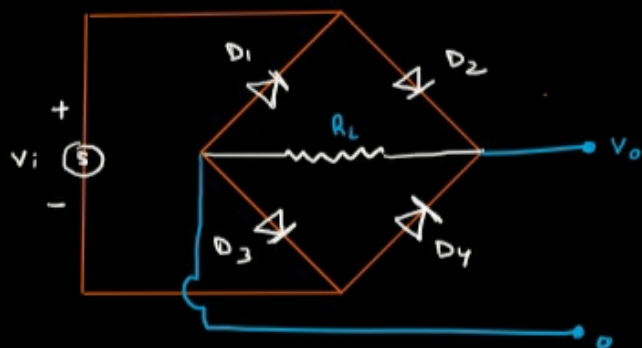


fb:

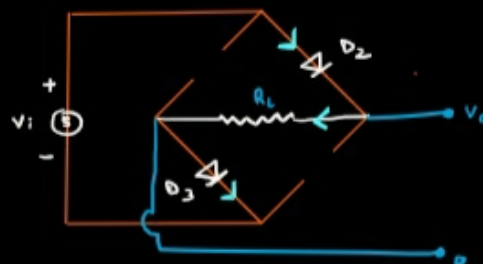


$$[v_i - v_{D_2} - v_{D_3} = v_o]$$



Rb:

(wrt \$D_2\$ & \$D_3\$)

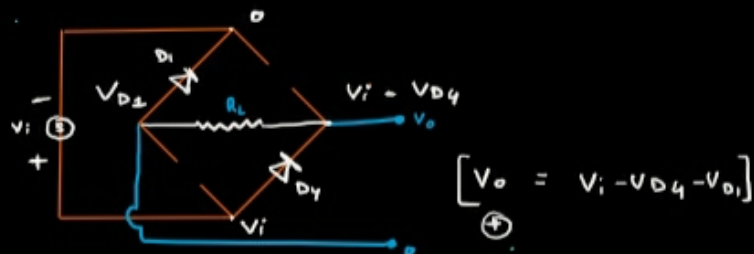

or Centre-tapping ↓

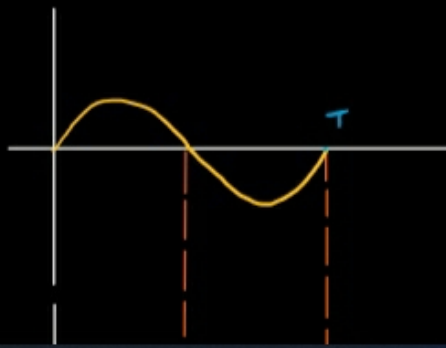

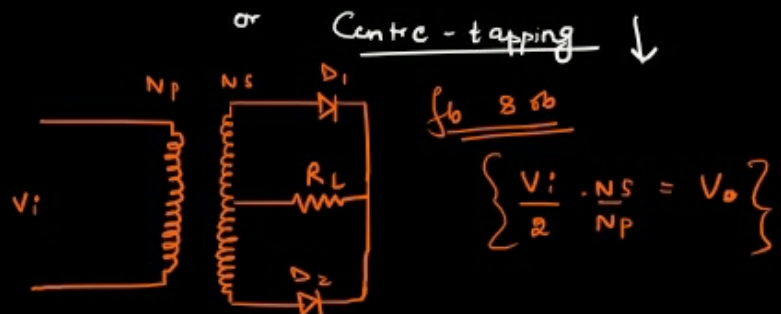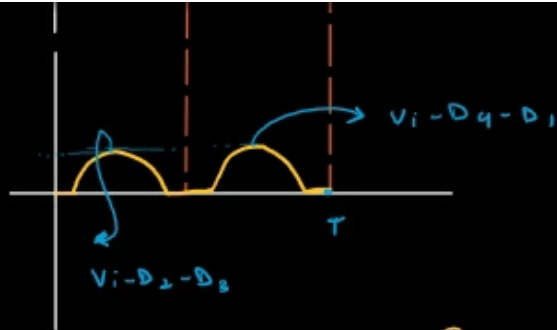



$$V = V_m$$

	Avg.	Rms.	FF $\frac{rms}{avg}$	$100 \sqrt{(ff)^2 - 1}$ Ripple %	$100/(ff)^2$ η
Half wave	V/π	$\frac{V}{2}$	$\pi/2$	121 %	40 %
Full wave	$2V/\pi$	$V/\sqrt{2}$	$\pi/\sqrt{2}$	48.34 %	81 %

* Clipper ckts: Used to clip either the positive or negative halves of V_i .


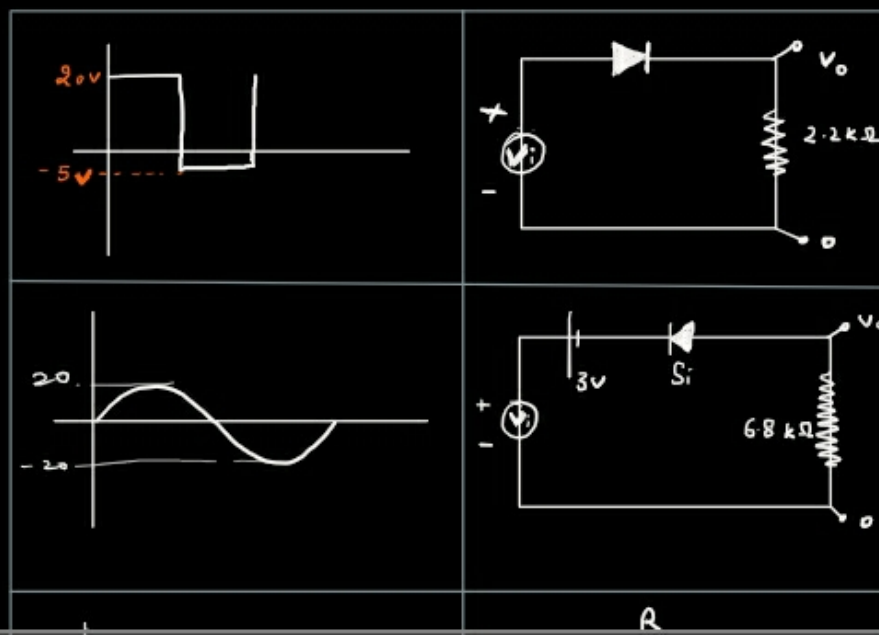
Q: Determine V_o if V_i is (a) & ckt is (b).



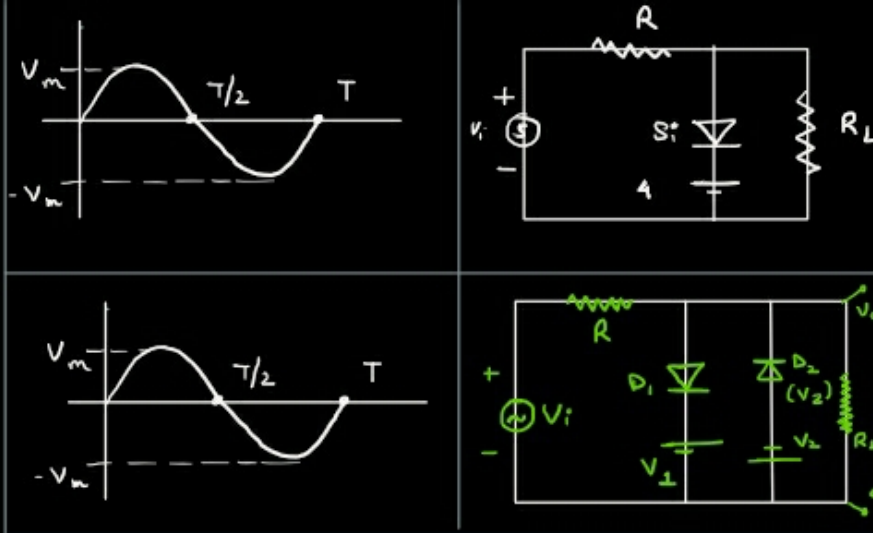


[Soln in register]

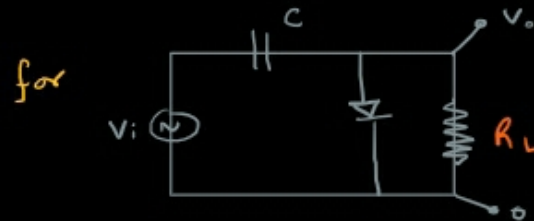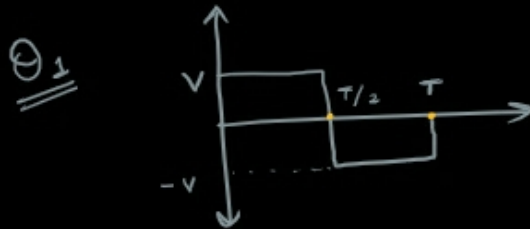* Clamper: It shifts the voltage graphs up or down by some units. $[e = RC \gg T/2]$




Sol: for $0 - T/2$

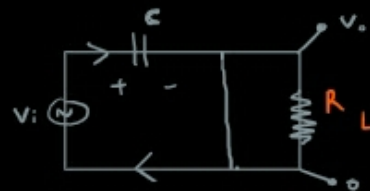

$$V_o = 0 \quad \{ i_L = 0 \}$$


$$V_C = + - | - = V_i = V$$

for $T/2 - T$

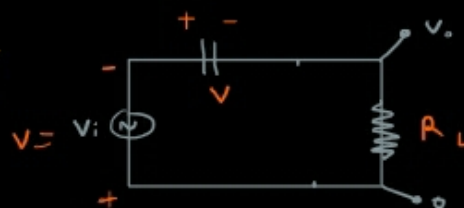


$$V_o + V + V = 0$$

$$V_o = -2V$$

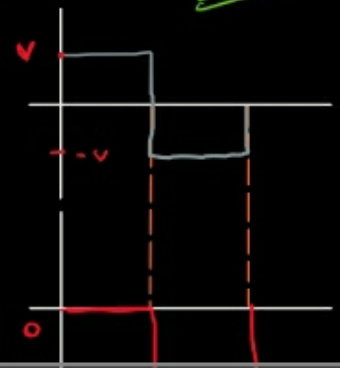

Sol:


for $0 - T/2$

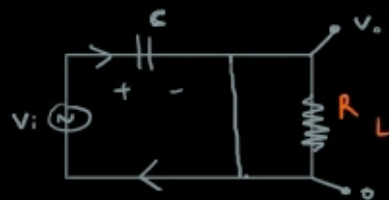

$$V_o = 0 \quad \{i_L = 0\}$$


$$V_C = + - | - = V_i = V$$

for $T/2 - T$

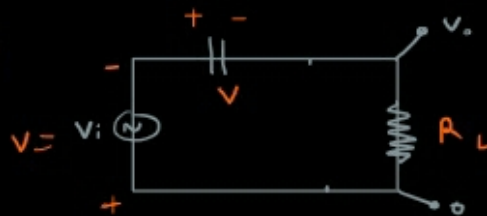


$$V_o + V + V = 0$$



$$V_o = -2V$$

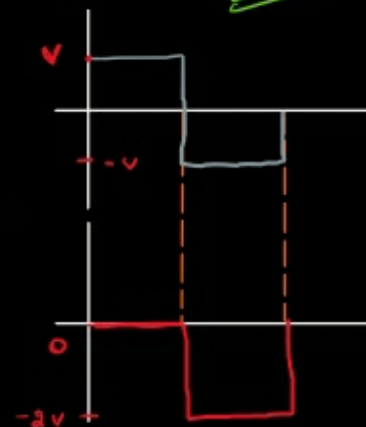

Q2:

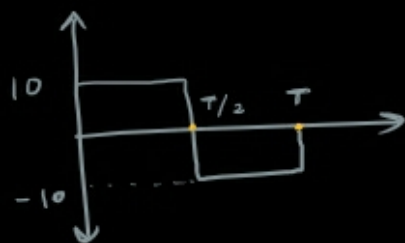


for

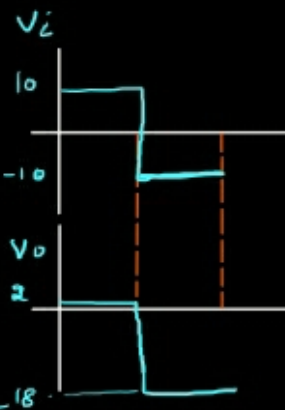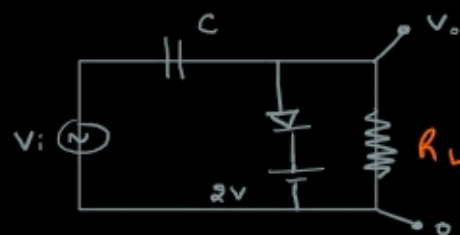


Sol:

for $0 - T/2$:

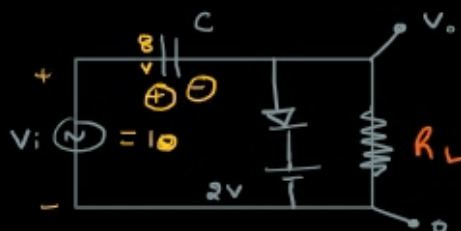

$$V_o = 2V$$

for $T/2 - T$

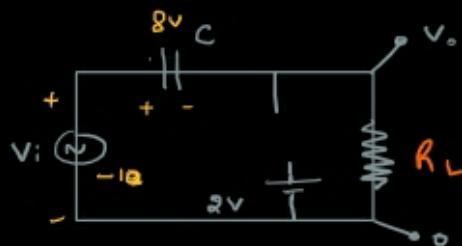

$$V_o = 18V$$