

28th Jan 22

Date
DELTA Pg No.

Unity gain for Inverting op-amp :-

$$\text{voltage gain} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

$$\text{If } R_f = R_i$$

$$\Rightarrow \boxed{\text{voltage gain} = -1}$$

Q. Design an inverting opamp with gain 10.


$$R_f = 10R_i$$

$$\text{voltage gain} = -\frac{R_f}{R_i} = -10$$


$$\text{Eg } V_o = ?$$

$$\begin{aligned} \text{If } V_o &= -\frac{R_f}{R_i} \times V_i \\ &= -\frac{500K}{100K} \times 2V \end{aligned}$$

$$\boxed{V_o = -10V}$$

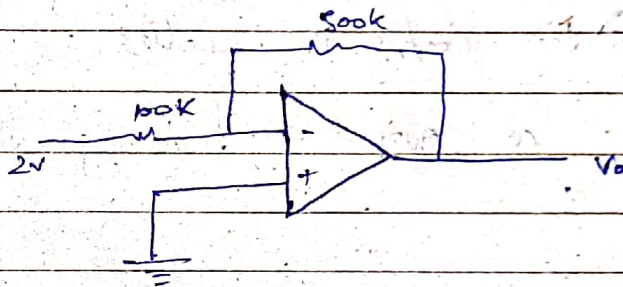

Non-Inverting config:-

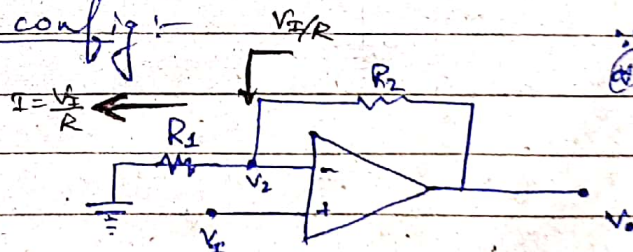

Resistance of op-amp = ∞ .

$$I = \frac{V_i}{R}$$

$$\Rightarrow \boxed{V_o = V_i + \left(\frac{V_i}{R}\right) R_2 = V_i \left(1 + \frac{R_2}{R_1}\right)}$$

Since + and - terminals are virtually short circuited
Hence $V_- = V_i$

$$G = \frac{V_o}{V_i} = \left(1 + \frac{R_2}{R_1} \right)$$

→ Gain for non-inverting config.


⊗ for unity gain :-

$$R_2 \rightarrow 0$$

$$G = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$


$$\Rightarrow \frac{V_o}{V_i} = 1$$

$$\Rightarrow \boxed{V_o = V_i}$$

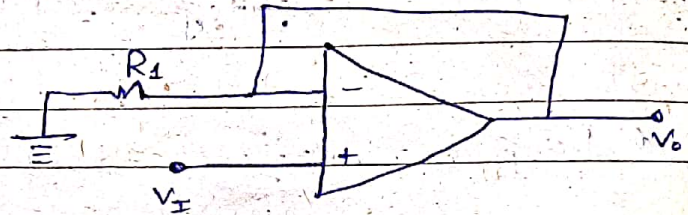

⊗ this config is called 'Unity follower'
 as output is following the input.

Q.

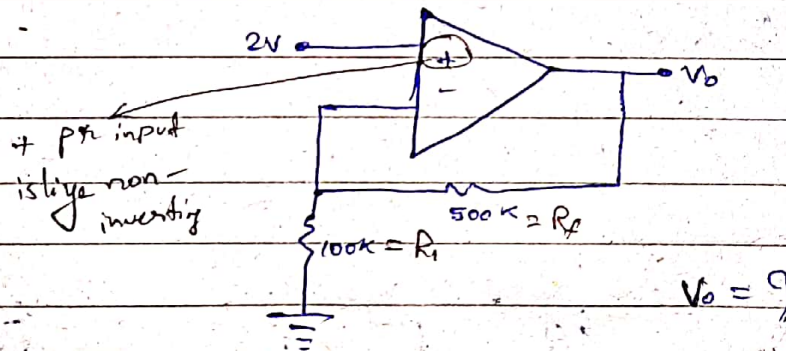


$$V_o = ?$$

Sol.

$$G = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$

$$V_o = \left(1 + \frac{500}{100} \right) (2V) = \boxed{12V} \text{ Ans}$$

SUMMING AMPLIFIER (Summer) :-

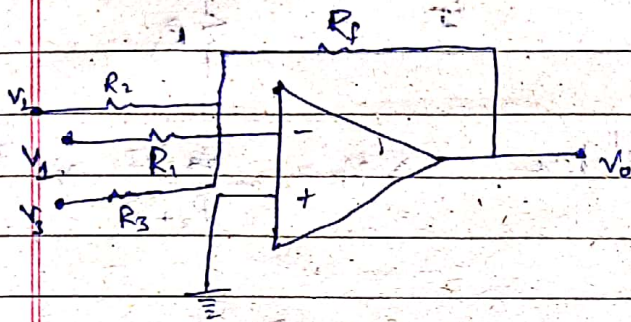

Both inverting and non inverting used together

$$V_0 = -\frac{R_f}{R_1} V_1 - \frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} V_3$$

$$\Rightarrow V_0 = -\left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right]$$

Q. Calculate V_0 ?

$$R_f = 1 \text{ M}\Omega, \quad V_1 = -2 \text{ V}, \quad V_2 = +3 \text{ V}, \quad V_3 = +1 \text{ V}$$


$$R_1 = 200 \text{ k}, \quad R_2 = 500 \text{ k}, \quad R_3 = 1 \text{ M}\Omega$$


$$\begin{aligned} V_0 &= -\left[\frac{10^6}{2 \times 10^5} \times (-2 \text{ V}) + \frac{10^6}{5 \times 10^5} \times 3 + \frac{10^6}{10^6} \times 1 \right] \\ &= -[3 - 10 + 6 + 1] = \boxed{3 \text{ V}} \text{ Ans} \end{aligned}$$

Difference Amplifier:-

due to V_{I1} $V_{O1} = -\frac{R_2}{R_1} \times V_{I1}$
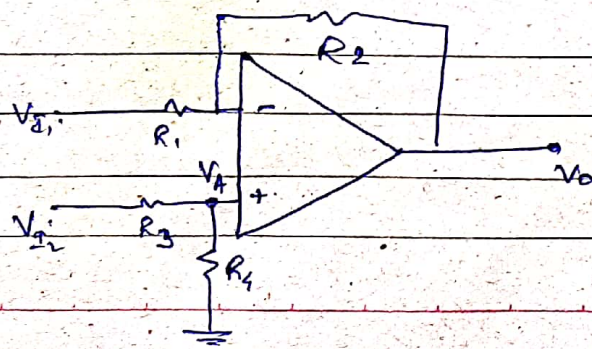
$$V_{O2} = \left(1 + \frac{R_2}{R_1} \right) V_{I2}$$



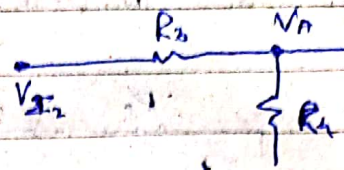

$$\Rightarrow V_{O2} = \left(1 + \frac{R_L}{R_1}\right) \left(\frac{R_1}{R_3 + R_4}\right) V_{I2} \quad \text{Put here} \Rightarrow V_A = \frac{V_{I2} \times R_4}{R_3 + R_4}$$

$$= \left(\frac{R_1 + R_2}{R_1}\right) \left(\frac{R_1}{R_3 + R_4}\right) V_{I2} \quad \left[\because \frac{R_4}{R_3} = \frac{R_1}{R_1} \right]$$

$$\Rightarrow V_{O2} = \left(\frac{R_2}{R_1}\right) V_{I2}$$

$$V_O = V_{O1} + V_{O2}$$

$$= -\frac{R_2}{R_1} V_{I1} + \frac{R_2}{R_1} V_{I2} = \frac{R_2}{R_1} (V_{I2} - V_{I1})$$

$$\Rightarrow \boxed{V_O = \frac{R_2}{R_1} (V_d)}$$

Simply find difference b/w the terminals.

Q.

V_2 and V_3 ?

