
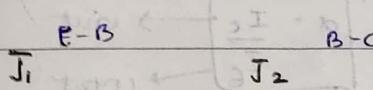
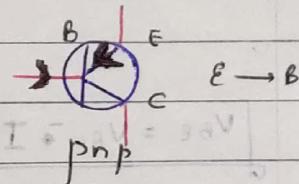
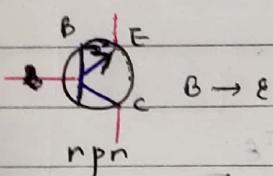



* Bipolar Junction Transistor

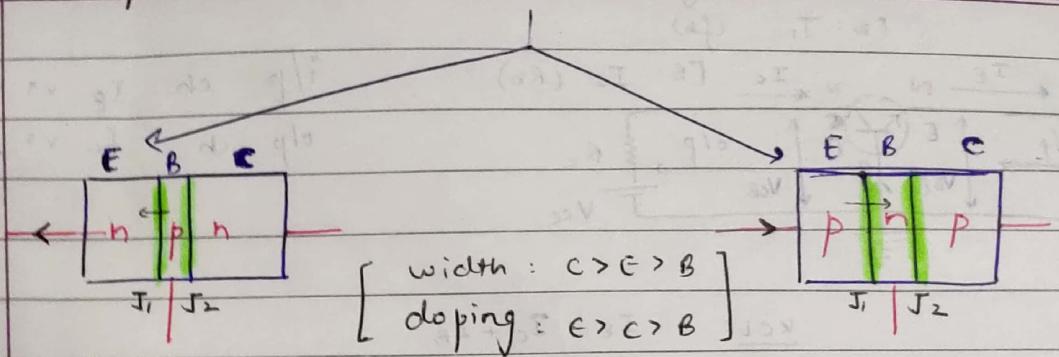

Region of op.


f. b.	r. b.	Active	Amplifier
f. b.	f. b.	Satn.	ON
r. b.	r. b.	Cut off	OFF
\approx f. b.	f. b.	Inverted	$E \leftrightarrow C$

* Transistor operⁿ (Active mode)

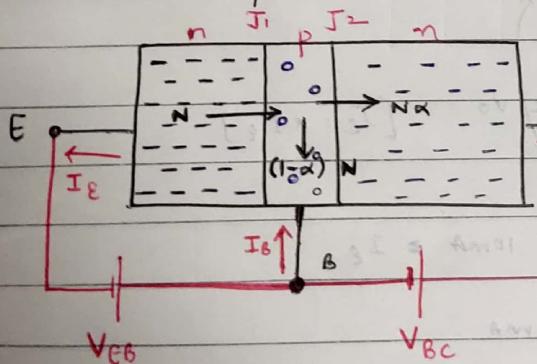


$\{ \alpha \approx 0.98 - 0.95 \}$
n: no of e⁻ flowing
 I_C : Satⁿ current

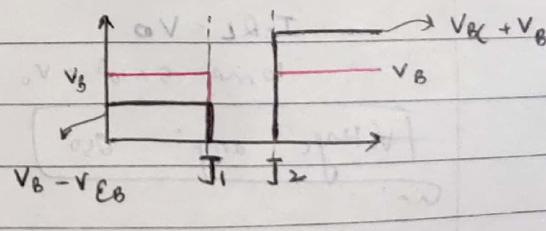v. as base region is
v. lightly doped & thin.




$$KCL: I_C + I_B = I_E$$

$$I_C = \alpha I_E + I_{C0}$$

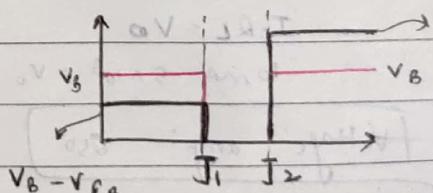

(CB)

Common Base configⁿ

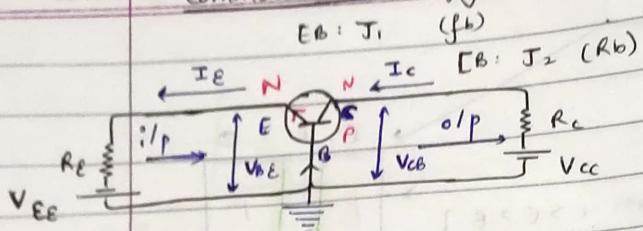

i/p ch: I_E vs V_{BE}
o/p ch: I_C vs V_{CB}

$$\text{KCL: } I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CO}$$



$$V_{BE} = V_{EE} - I_E R_E$$

$$\text{also } I_C \approx \alpha I_E$$

$$\text{as } I_{CO} \approx 0$$

$$V_{CB} = V_{CC} - I_C R_C$$
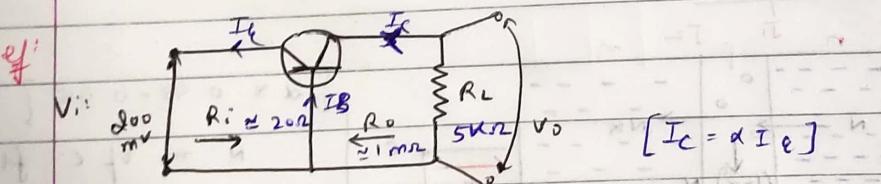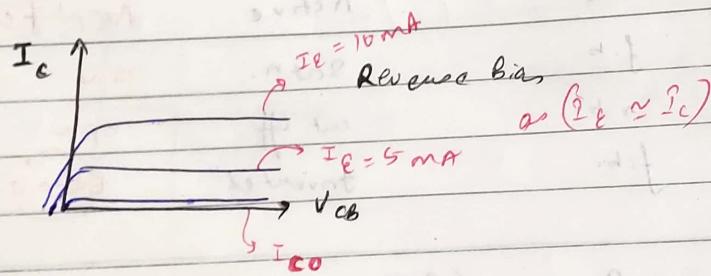
$$\begin{cases} \alpha = \frac{I_C}{I_E} \rightarrow \text{out} \\ \text{in} \end{cases}$$



$$\frac{200 \text{ mV}}{20 \Omega} = \text{Input} = I_E = 10 \text{ mA} = I_C$$


$$I_E \approx I_C \approx 10 \text{ mA}$$

$$I_C R_L = V_o$$

$$10 \text{ mA} \cdot 5 \times 10^3 = V_o = 50 \text{ V}$$

$$\boxed{\text{Voltage amp: 250}}$$


CE

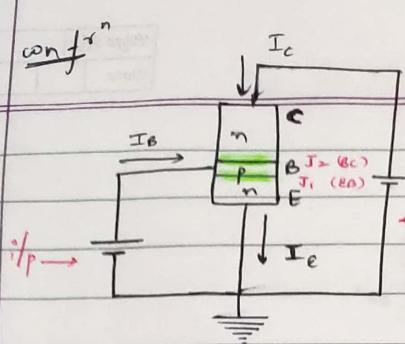

$$I_E = I_C + I_B$$

Page No.	
Date	

$$I_C = \alpha I_E + I_{CBO}$$

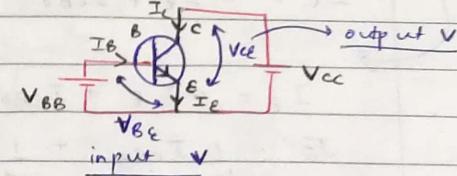


$$\beta = \frac{I_C}{I_B} \quad \alpha = \frac{I_C}{I_E}$$

also

$$I_C = \beta I_B + (\beta + 1) I_{CBO}$$

$$\frac{I_C}{\beta} + I_C = \frac{I_C}{\alpha} \quad \frac{1}{\beta} + 1 = \frac{1}{\alpha}$$

also

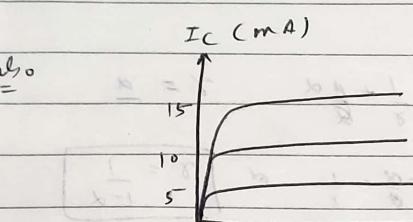

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\frac{\beta}{\beta+1} = \alpha$$



$$\beta = \frac{\Delta I_C}{\Delta I_B} = \frac{5}{0.1} = 50$$

I_C is output current


$$V_{CE} = V_{CC} - I_C R_L$$

$$V_{BE} = V_{BB} - I_B R_B$$

CC config

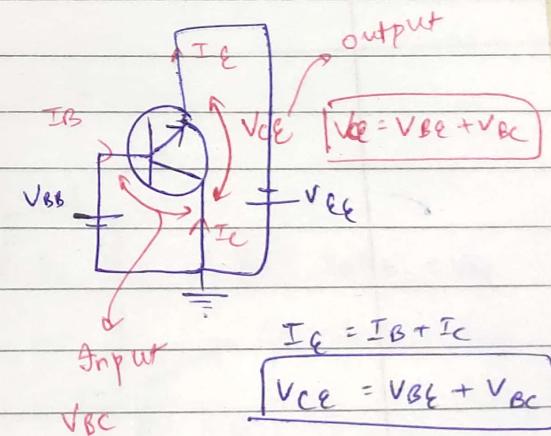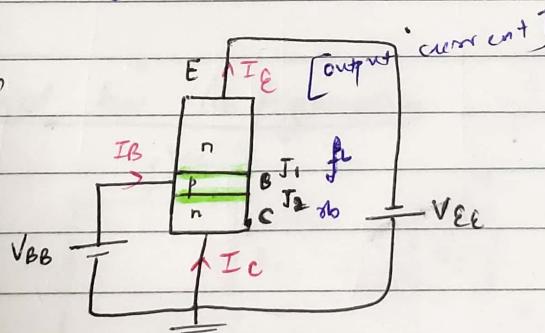

$$\text{now } I_C = \alpha I_E$$

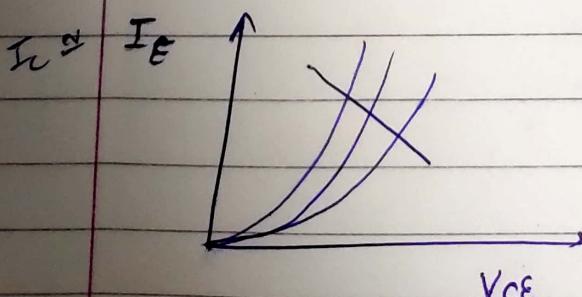

o/p of CE \approx o/p of CC

$$\gamma = \frac{I_E}{I_B} \approx \frac{\Delta I_E}{\Delta I_B}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = \alpha I_E + I_{CBO} + I_B$$

$$I_E = \frac{1}{1-\alpha} I_{CBO} + \frac{1}{1-\alpha} I_B$$

$$\boxed{I_E = \gamma [I_{CBO} + I_B]}$$

$$\gamma = \frac{I_E}{I_B} \quad \beta = \frac{I_C}{I_B} \quad \alpha = \frac{I_E}{I_E}$$

$$I_E = I_B + I_C$$

$$I_E = \frac{I_E}{\gamma} + \frac{I_E}{\gamma} \alpha \quad 1 = \frac{1}{\gamma} + \frac{\alpha}{\gamma} \quad \gamma = \frac{1}{1-\alpha}$$



$$I_B \cdot \gamma = I_B + I_B \beta \quad 1 - \alpha = \frac{1}{\gamma} \quad \therefore \boxed{\gamma = \frac{1}{1-\alpha}}$$

$$\boxed{\gamma = \beta + 1}$$

$$\boxed{\beta = \frac{\alpha}{1-\alpha}}$$

$$AC = 5V$$

$$AB = 5V - 33V = -28V$$

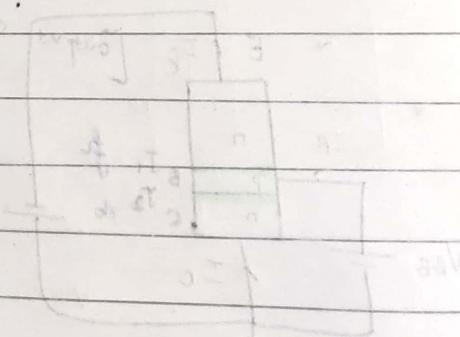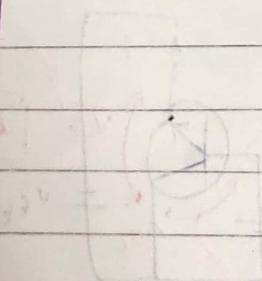

input



out



Page No. _____
Date _____

DC Biasing of Transistors

npn [CE]

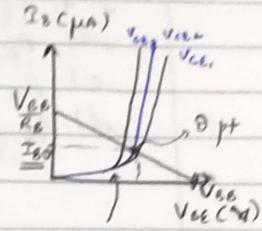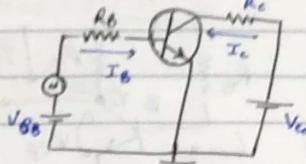

input

also DC:

$$V_{BB} - (I_B R_B) = V_{BE}$$

$$\left[\frac{V_{BB}}{R_B} - \frac{V_{BE}}{R_B} = I_B \right]$$


output

$$V_{CC} - I_C R_C = V_{CE}$$

$$\left[\frac{V_{CC}}{R_C} - \frac{V_{CE}}{R_C} = I_C \right]$$

$$\text{if } V_{CE_1} > V_{CE_2} > V_{CE_3}$$

I_C (mA)


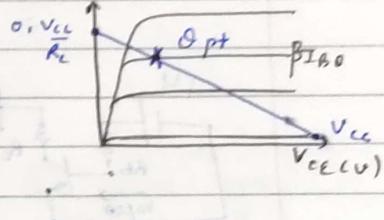


* Operating pt must be selected in centre of active region
[for no distortion]

$$\text{also } I_C = \beta I_B + (\beta + 1) I_{CB0}$$

TIP $\rightarrow I_{CB0} \uparrow I_C \uparrow$

Fixed Bias Configuration

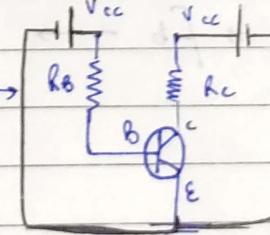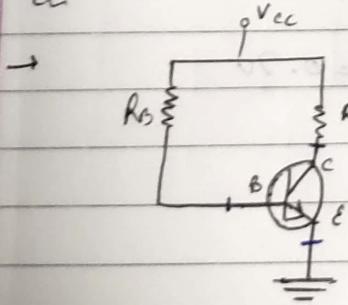

$$V_{CC} - I_B R_B = V_{BE}$$

$$V_{CC} - I_C R_C = V_{CE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$I_C = \beta \left(\frac{V_{CC} - V_{BE}}{R_B} \right)$$


Q: for fixed-bias common-emitter find

a) I_C

b) R_C

c) R_B


d) V_{CE}

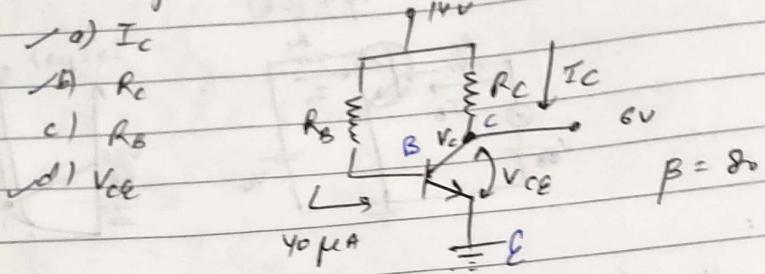

$$I_B = 40 \mu A$$

$$I_C = 80 \times 4 \times 10^{-5} A$$

$$= 3.2 \times 10^{-3} = 3.2 mA$$

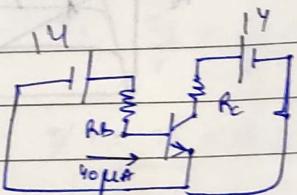

$$\frac{13.3 \times 10^6}{40} = R_B$$

$$14 - (40 \mu A) R_B = V_{BE}$$

$$14 - (3.2 mA) R_C = 6V = V_C = V_{CE} = V_C - V_E$$


$$\textcircled{2} \quad \beta = \frac{(3.2 \text{ mA}) R_C}{10}$$

$$\boxed{2.5 k\Omega = R_C}$$

$$\text{also } V_{BE} \rightarrow f_b \rightarrow V_{BE} = 0.7V$$



Page No.	
Date	

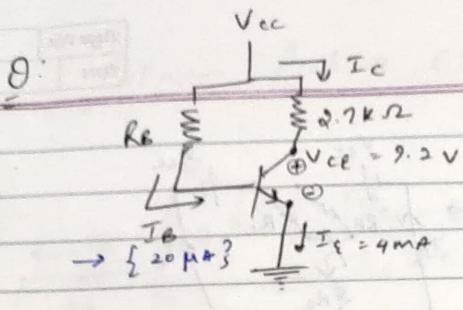

Find:
 a) β
 b) V_{ce}
 c) β
 d) R_B

Sol: $I_e \approx I_c \approx 4 \text{ mA} \quad \text{--- (a)}$

$$V_{ce} = (2.7 \times 10^3) (4 \times 10^{-3}) = 7.2 \text{ V}$$

$$V_{ce} = 10.8 = 7.2 \text{ V}$$

$$\boxed{V_{cc} = 18 \text{ V}} \quad \text{--- (b)}$$

$$18 - I_B R_B = 0.7 \text{ V}$$

$$\boxed{17.3 = I_B R_B} \quad \text{--- (c)}$$

$$\boxed{\beta_B = \frac{4 \text{ mA}}{\beta}}$$

$$\boxed{\frac{17.3}{4} = \frac{R_B}{\beta}}$$


$$5.26 \times 10^{-6} = \frac{4 \times 10^{-3}}{\beta}$$

$$\boxed{\beta = 200}$$

$$R_B = 17.3 \times 50$$

$$R_B = 173 \times 5 = 865 \Omega$$

Emitter-Bias configⁿ

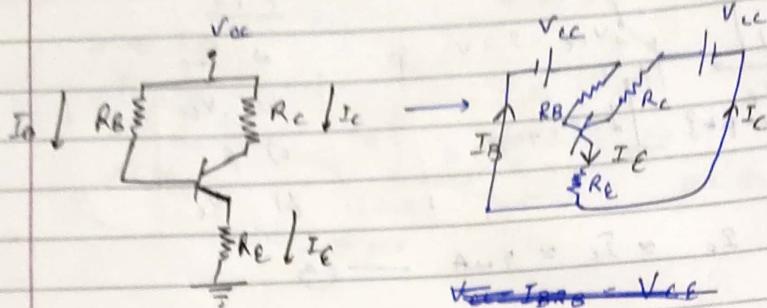

$$V_{BE} = I_B R_B = V_{CE}$$

$$V_{CE} = I_C R_C = V_{EE}$$

$$I_E = \gamma I_B$$

$$V_{CE} - I_B R_B - I_E R_E = V_{BE}$$

$$V_{CE} - I_C R_C - I_E R_E = V_{EE}$$

$$I_E = (\beta + 1) I_B$$

$$V_{CE} - [R_B + (\beta + 1) R_E] I_B = V_{BE}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$\beta \ll (\beta + 1) R_E$$

$$V_{CC} - I_C (R_C + R_E) = V_{CE}$$

$$I_C \approx \frac{[V_{CC} - V_{BE}]}{R_C}$$

$$I_C = \beta I_B$$

Q: for Emitter-bias det:

- a) R_C ✓
- b) R_E ✓
- c) R_B ✓
- d) V_{CE} ✓
- e) V_B

$$8.9 = \frac{3 \times 10^3}{80} R_E$$

$$(R_B = \frac{30}{80} \times \frac{80 \times 8}{5}) =$$


$$R_B = \frac{2.4 \times 10^5}{80} \Omega$$

$$\frac{80}{81} \cdot \frac{\beta}{1+\beta}$$

$$I_B = \frac{3 \text{ mA}}{80}$$

$$I_C \approx I_E$$
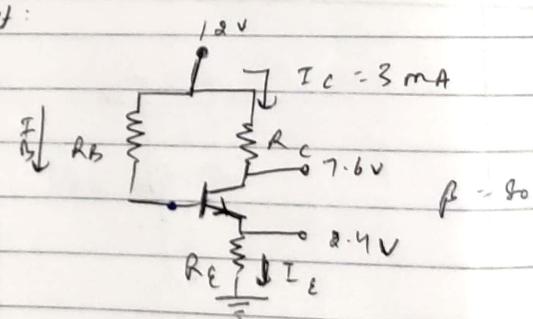
$$\frac{81}{80} \times 3 \text{ mA} = I_E = \frac{243}{80} \text{ mA}$$



$$12 - I_B R_B = 3.1 \text{ V} = V_B$$

$$12 - (\beta \times 10^{-3}) R_C = 7.6 \text{ V} \rightarrow R_C = \frac{4.4 \times 10^3}{3} \Omega$$

$$R_E = \frac{2.4 \times 80 \times 10^3}{243} \Omega = 1.366 \text{ k}\Omega$$

$$R_E = 800 \Omega$$

V_{BE}

V_{CE}

$V_{BE} = 0.7$

$V_B = 80$

$V_{CE} = 7.6$

$I_C = 3$


I_C



V_{BQ}

Collector Feedback Biasing

Page No. _____
Date _____

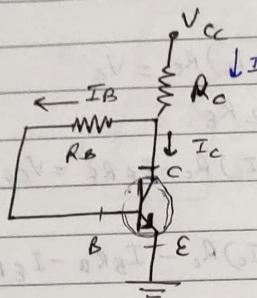

$$V_{CC} - I_R C = V_{CE} \quad \text{as } V_E = 0$$

$$V_{CC} - I_R C - I_B R_B = V_B = V_{BE} \quad \text{as } V_E = 0$$

$$V_{CC} - (I_B + I_C) R_C = V_{CE} \quad \text{--- (i)}$$

$$V_{CC} - (I_B + I_C) R_C - I_B R_B = V_{BE} \quad \text{--- (ii)}$$

$$I_C = \beta I_B$$

$$V_{CC} - V_{CE} = I_B \quad \leftarrow \quad V_{CC} - (\beta + 1) I_B R_C = V_{CE} \quad \text{--- (i)}$$

$$(\beta + 1) R_C \quad V_{CC} - (\beta + 1) I_B R_C - I_B R_B = V_{BE} \quad \text{--- (ii)}$$

or

$$\frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + R_B} = I_B \quad \left[I_C = \beta \left\{ \frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + R_B} \right\} \right]$$

Advantage & point: Against varies to T.


a. $\sim \sim \sim \sim V_{CC}$

b. $\sim \sim \sim \sim \beta$

Disadvantage : 1. $R_C \uparrow \uparrow$ $V_{CC} \uparrow \uparrow$ cos ↑
 $R_B \downarrow \downarrow$ R_b of c-B ↓

$$V_{CC} = 20V$$

θ :

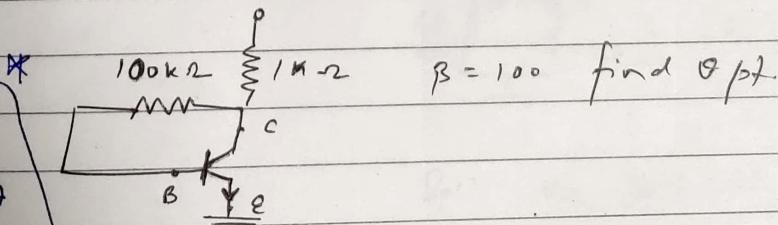

$$V_{BE} = 0.7V$$

$$V_B = 96.01 \mu A$$

$$V_{CE} = 10.30V$$

$$I_C = 9.601 \mu A$$

$$I_C = 100 I_B$$

$$96.01 \mu A = I_B$$

$$\frac{19.3}{201} \mu A = I_B$$

$$20 - (I_C + I_B) 10^3 = V_{CE}$$


$$20 - (I_C + I_B) 10^3 - I_B (10^5) = V_{BE}$$

$$20 - (101) 10^3 I_B = V_{CE}$$

$$20 - [(101) 10^3 + 10^5] I_B = V_{BE} = 0.7V$$

Collector feedback Biasing with Emitter Resistance

Page No. _____
Date _____

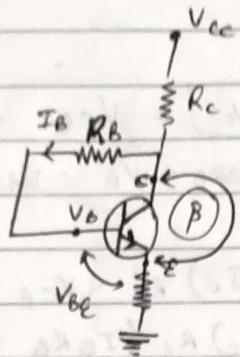

$$V_{CC} - (I_B + I_C)R_C = V_C$$

$$V_E = I_E R_E$$

$$V_{CC} - (I_B + I_C)R_C - I_E R_E = V_{CE} \quad (i)$$

$$V_{CC} - (I_B + I_C)R_C - I_B R_B - I_E R_E = V_{BE}$$

L6(j)

$$(I_E \approx I_C)$$

$$I_B \beta = I_C$$

$$\text{[Values]} \quad V_{CC} - V_{CE} = [\beta + 1] R_C + \beta R_E I_B$$

$$\frac{V_{CC} - V_{BE}}{(\beta + 1) R_C + \beta R_E + R_B} = I_B$$

$$\beta I_B = I_C = I_E = \frac{\beta [V_{CC} - V_{BE}]}{(\beta + 1) R_C + \beta R_E + R_B}$$

$V_{BE} =$


V_A

V_f

Δ

Voltage-Divider Bias Configuration

Page No. _____
Date _____

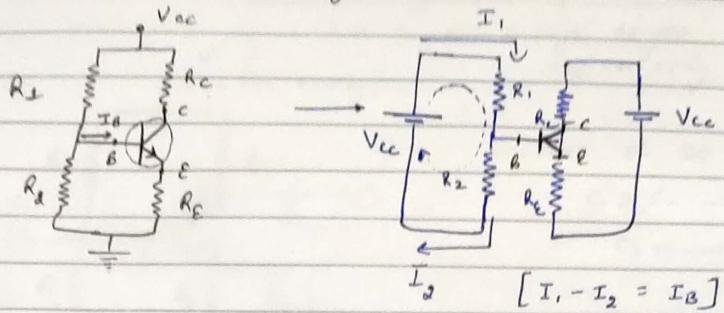

$$V_{CC} - I_1 R_1 - I_2 R_2 = 0$$

$$\boxed{V_B = I_2 R_2 = V_{CC} - I_1 R_1} \quad (i)$$

$$(ii) \boxed{V_{BE} = V_{CC} - I_1 R_1 - I_E R_E} \quad | V_E = I_E R_E$$

$$V_{CC} - I_C R_C = V_C$$

$$(iii) \boxed{V_{CC} - I_C R_C - I_E R_E = V_{CE}}$$

Find:

a) I_C

b) V_E

c) V_{CC}


d) V_{CE}

$$V_{BE} = 0.7V$$

$$V_Q = 1.2V$$

$$V_B = 1.9V$$

$$f) R_1$$

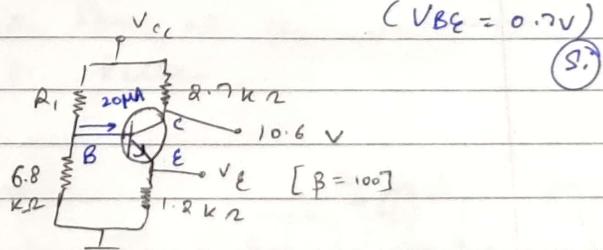

$$SOL: V_{CC} - (0.7 \times 10^3) I_C = 10.6$$

$$I_B = 20 \mu A \quad I_C = 2 mA$$

$$V_{CC} = 10.6 + 5.4$$

$$V_E = 2 \times 10^{-3} \times 1.2 \times 10^3 * \boxed{V_{CC} = 16 V}$$

$$\boxed{V_E = 24 V} \quad \boxed{V_{CE} = 16 - V_E}$$

Q) $100 I_B = I_C \approx I_E$

$$16 - R_1 I_1 = V_B$$

$$16 = R_1 I_1 + (6.8 \times 10^3) I_2 \quad I_2 \cdot 6.8 k\Omega = V_B$$


$$R_1 I_1 + 6.8 \times 10^3 I_2 = 16 \quad \boxed{V_{CE} = 13.6 V}$$

$$(6.8 \times 10^3) I_1 + 6.8 \times 10^3 I_2 = 136 \times 10^{-3}$$

$$(R_1 - 6.8 \times 10^3) I_1 = 15.964$$

AC response or Small Signal Analysis of BJT

Page No. _____
Date _____

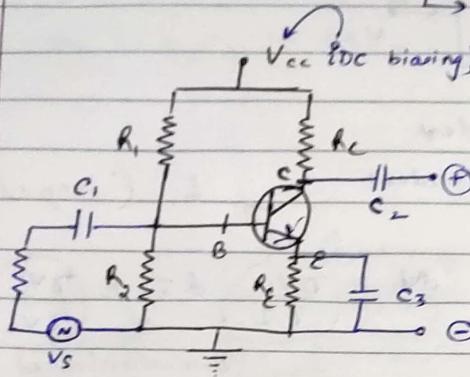

Small enough to get Qpt in active region only

in case of DC

C_1 & C_2 \rightarrow Coupling cap.
 C_3 \rightarrow By pass cap.

$$X_C = \frac{1}{\omega C} \text{ or } \frac{1}{2\pi f C}$$

for DC $\rightarrow f=0 \quad X_C = \infty$
AC $\rightarrow f \neq 0 \quad X_C \neq \infty$

(gen) $X_C \rightarrow$ small
 $\approx f$ changes

(short ckt)

$$\therefore X_C \approx 0$$

thus I_E goes via C_3
not R_E

(short ckt)

to find AC rep:

i) ac eqv ckt find

ii) replace the transistor with eg models



eqv. ckt.

~~AC eqv ckt~~


1. Short ckt all DC source $V=0$

2. Short all the caps. $\cdots \cdots$


3. Redraw.

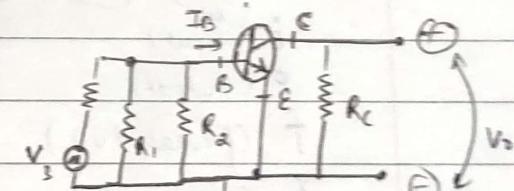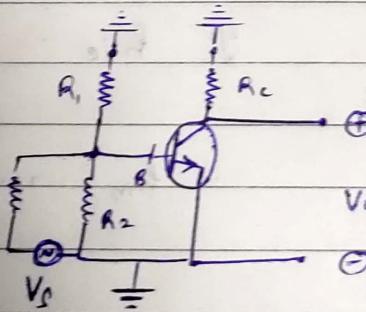

Eq model of Transistor \Rightarrow

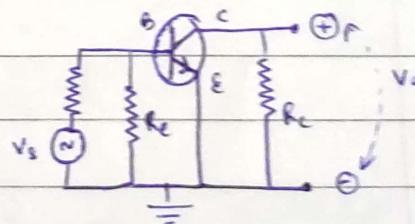

Hybrid Model Ch-model

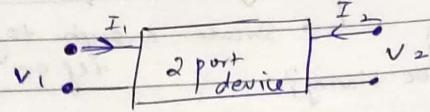

$V_1 \propto I_2 \rightarrow$ dependent
 $V_2 \propto I_1 \rightarrow$ independent

h_{11} (impedance)

$$V_1 = f_1(I_1, V_2) \rightarrow dV_1 = \frac{\partial V_1}{\partial I_1} dI_1 + \frac{\partial V_1}{\partial V_2} dV_2$$

$$I_2 = f_2(I_1, V_2) \rightarrow dI_2 = \frac{\partial I_2}{\partial I_1} dI_1 + \frac{\partial I_2}{\partial V_2} dV_2$$

dimensionless

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

admittance (h_{22})

$$\left. \frac{V_1}{i_1} \right|_{V_2=0} = h_{11} \quad \text{and} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{i_1=0}$$

$$\left. \frac{i_2}{i_1} \right|_{V_2=0} = h_{21} \quad \text{and} \quad h_{22} = \left. \frac{i_2}{V_2} \right|_{i_1=0}$$


Nomenclature:

i (input)	e	e
\circ (output)	cE for e	h_{ie} : input impedance of cE .
f (forward vol.)	$CB \rightarrow b$	h_{re} : rev. voltage of CB
r (rev. vol.)	$CC \rightarrow c$	


$$v_1 = h_i i_1 + h_{f2} v_2 \rightarrow (i)$$

$$v_{ir} = h_f i_1 + h_o v_2 \rightarrow (ii)$$


Revenue KVL

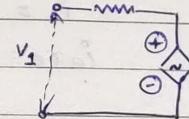

Rev.
KCL

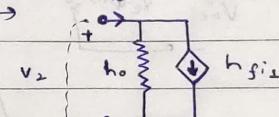

Combining

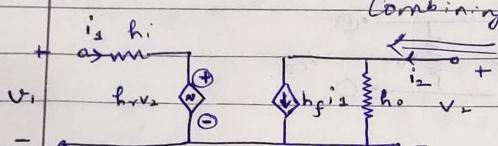


$$\underline{\text{CE}}: h_i \rightarrow h_{ie} \quad i_1 \rightarrow i_{eb}$$

$$h_f \rightarrow h_{fe} \quad v_1 \rightarrow v_{be}$$

$$h_o \rightarrow h_{oe} \quad v_{ir} \rightarrow v_{ce}$$
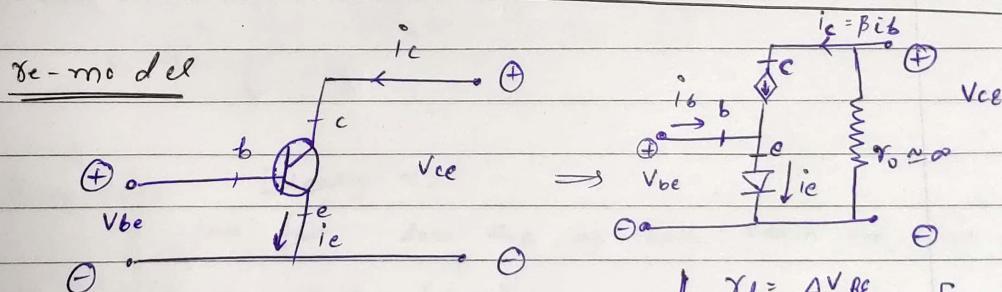
$$h_r \rightarrow h_{re} \quad v_2 \rightarrow v_{ce}$$



What is r_e ?

$$r_d = \frac{\Delta V_{BE}}{\Delta I_B}$$

$$\frac{I_D}{I_D}$$

$$I_D = I_S \left(e^{\frac{V_D}{nV_T}} - 1 \right)$$


$$\Rightarrow T = 300K \quad n = 1$$

$$\gamma r_d = \frac{d I_d}{d V_d} = I_S \cdot \frac{d}{d V_d} \left(e^{\frac{V_D}{300} \cdot 11600} - 1 \right)$$

$$\gamma r_d = I_S \cdot e^{\frac{V_D}{V_T}} = \frac{I_S + I_D}{V_T} \quad I_S \ll I_D$$



$$\frac{1}{r_d} \approx \frac{I_D}{V_T}$$
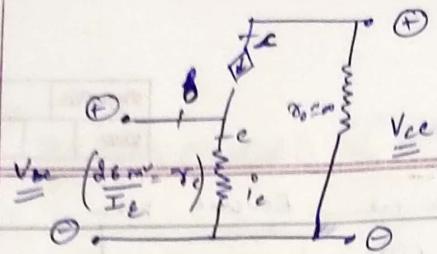
$$\boxed{r_d = \frac{26 \text{ mV}}{I_D} \text{ or } \gamma r_d = \frac{26 \text{ mV}}{I_D}}$$






$$V_{be} = \left(\frac{d\sigma m}{I_E} - r_o \right) i_e$$
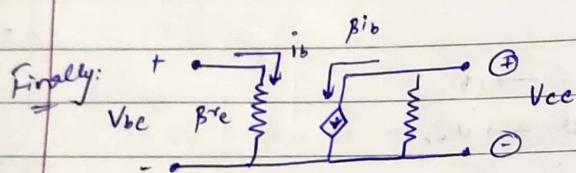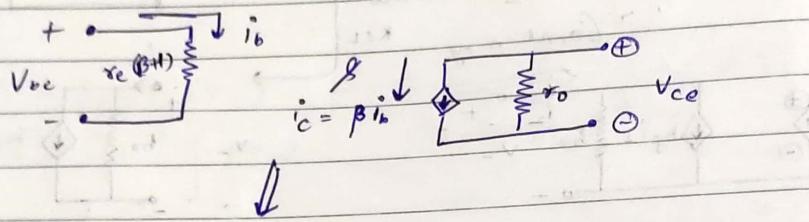
$$i_e r_o = (\beta + 1) r_o \cdot i_B = [(\beta + 1) r_o] \cdot i_B$$




Operational Amplifier

Page No. _____
Date _____

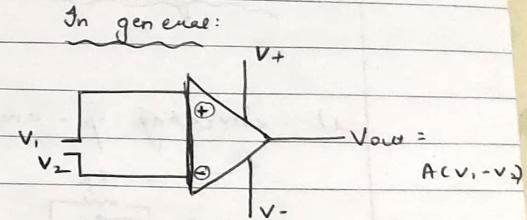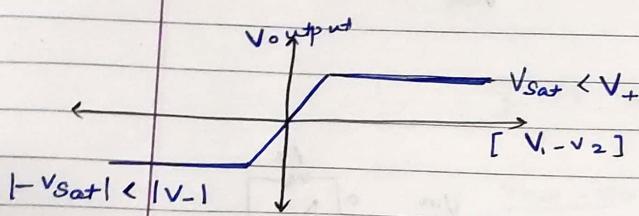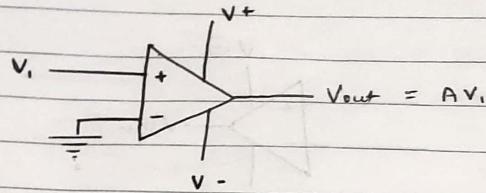

Equivalent circuit: (Ideal op-amp $\rightarrow R_i = \infty$)

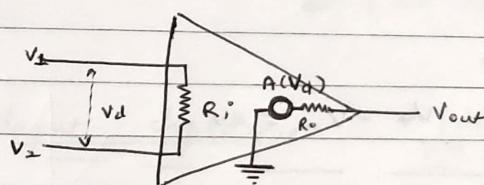$R_o = 0$
Bandwidth $= \infty$
 $A = \infty$



* Slew rate: [Ideally: ∞]

How fast does the op-amp reach the max voltage

given: [Volt / μ s]

* CMRR : $\frac{A_d}{A_c}$ [Ideally: ∞]

→ Practical

R_i MΩ

R_o Ω


A $10^5 - 10^6$

when $V_{in} = 0$ $mV \rightarrow V_{out}$


Slew rate $0.5 \text{ V}/\mu\text{s}$

CMRR $70 - 90 \text{ dB}$

* feedback op-amp

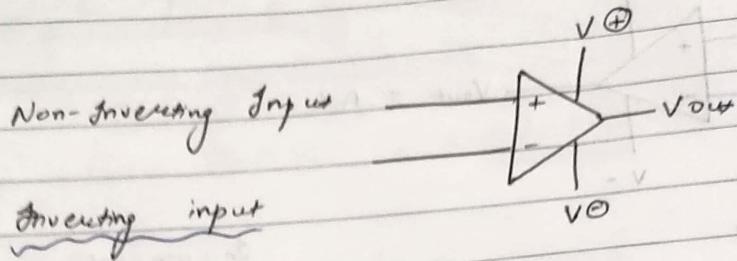

i) inverting op-amps

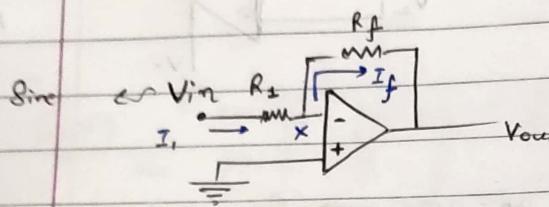

$$\text{eg: } A_{OL} = 10^6$$

$$V_{out} = A \cdot V_d$$

$$10 \mu V = V_d = V_+ - V_- \approx 0V$$

$$I_1 = \frac{V_{in}}{R_1}$$

& we know the resistance of diode is very high

$$I_f = \frac{V_{out}}{R_f} \quad \text{thus no current goes in them}$$



$$\frac{V_{in}}{R_1} = I_1 = I_f = \frac{V_{out}}{R_f}$$

$$V_d = -V_{in}$$

$$\left\{ \frac{V_{out}}{V_{in}} = \frac{R_f}{R_1} = A \right\}$$

Inverted

V_{in}

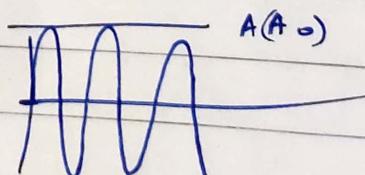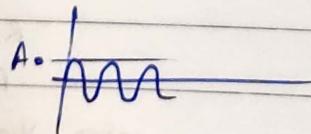


$$Z_{in} = \frac{V_{in}}{A \cdot V_{in}} = \frac{1}{A}$$


ii)

Non-inverting op-amp

Brief derivation

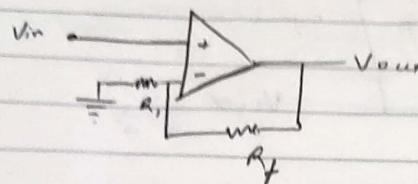

Virtual short
in
Linear region

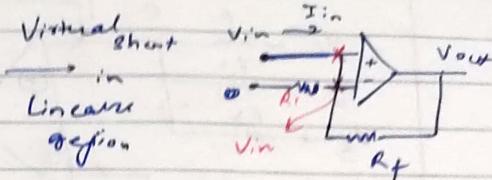

$$I_f = \frac{V_{out} - V_{in}}{R_f} \quad (\rightarrow)$$

$$I_f = I_2 \text{ as } I \text{ (op-amp)} \approx 0 \quad I_2 = \frac{V_{in}}{R_1} \quad (\rightarrow)$$

$$\left[\frac{V_{out} - V_{in}}{V_{in}} = \frac{R_f}{R_1} = \frac{V_{out} - 1}{V_{in}} \right]$$

$$\left[\frac{R_f + R_i}{R_i} = \frac{V_{out}}{V_{in}} = \frac{R_f + 1}{R_i} = A \right]$$

✓ [No-Inversion]

Same phase

Input Impedance:


$$\underline{V_{in}} = Z_{in}$$

$$I_{in}$$

$$I_{in} \approx 0$$

$$\left[\frac{V_{in}}{I_{in}} \approx \infty = Z_{in} \right]$$


f

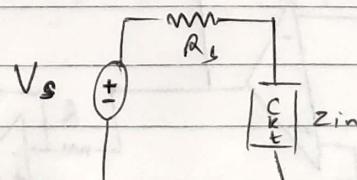

$$\left[\frac{V_s}{R_g + Z_{in}} = V_{in} \right]$$

Non-inverting thus if $Z_{in} \approx \infty$ then $V_{in} = V_s \rightarrow$ Better
but if $Z_{in} \approx R_g \rightarrow \frac{V_{in}}{2} \approx \frac{V_s}{2} \rightarrow$ Nope

* Summing Amplifier

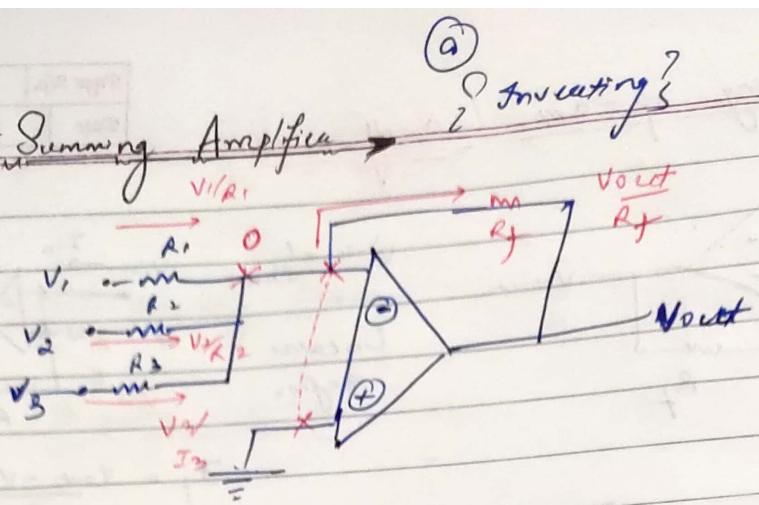

$$\left[\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = V_n \right]$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{V_{out}}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$


[Inverted]

$$V_{out} = \sum \frac{R_f}{R_i} (V_i)$$


Application of Summing Amp.

- > Providing DC offset
- > Digital to Analog converter
- > Audio Mixer

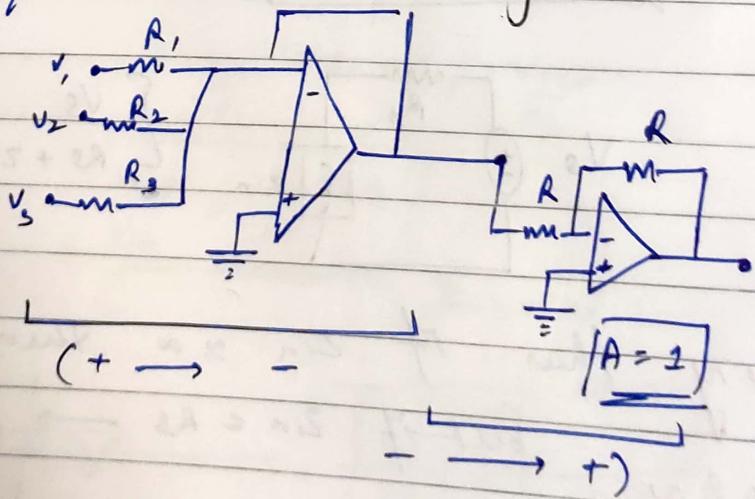→ Also you can do: (for inverting problem)



* Non-inverting summing amp

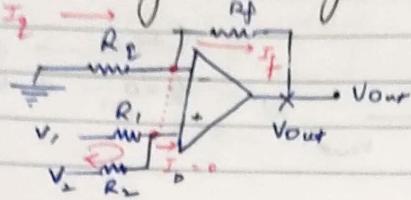

$$V_i - I_1 R_1 - I_2 R_2 = V_L$$

$$V_i - V_L = I_1 R_1 + I_2 R_2$$

$$[I_1 = I_2] \text{ as } I_o \approx 0$$

$$\left[\frac{V_i - V_L}{R_1 + R_2} = \underline{\underline{I_1}} = I_2 \right]$$

$$V_x - V_{out} = I_f R_f$$

$$V_i - I_1 R_1 = V_x = I_g R_g = V_{out} + I_f R_f$$


$$V_i - \left(\frac{V_i - V_L}{R_1 + R_2} \right) R_1 = I_g R_g = V_{out} + I_f R_f$$

$$I_f = I_g$$

$$V_i - \left(\frac{V_i - V_L}{R_1 + R_2} \right) R_1 = V_{out} + I_g R_f = I_g R_g$$


$$\left(\frac{V_i - V_{out} - \left(\frac{V_i - V_L}{R_1 + R_2} \right) R_1}{R_f R_f} = I_g = \frac{V_i}{R_g} - \frac{\left(\frac{V_i - V_L}{R_1 + R_2} \right) R_1}{R_g} \right)$$

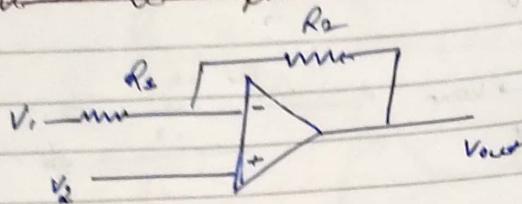* Differential op-Amp or Subtractor op-amp



Case 1 Case 2
 $V_o = 0$ $+V_i = 0$


Superposition theorem

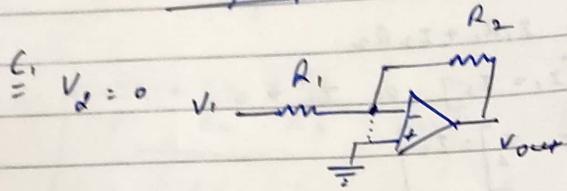

$$\frac{V_1}{R_1} = \frac{V_{out}}{R_2}$$

or

$$V_{out} = V_1 \frac{R_2}{R_1}$$

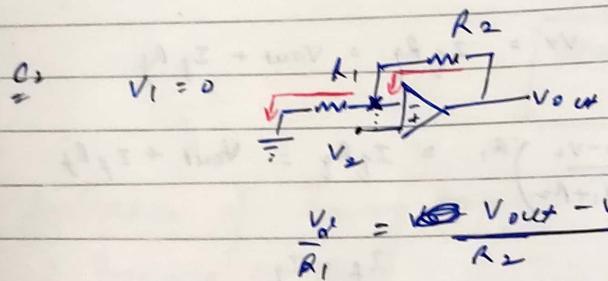

$$\frac{V_{out}}{V_2} = \frac{1}{R_1 + R_2}$$


$$V_{out} = \frac{V_2 R_2}{R_1 + R_2}$$

$$V_{out} = V_{o1} + V_{o2}$$


$$V_{out} = V_1 \frac{R_2}{R_1} + V_2 \frac{R_2}{R_1 + R_2} = \frac{(V_2 + V_1) R_1 R_2 + V_1 R_2^2}{(R_1 + R_2) R_1}$$


Impedance is low here.

for higher:

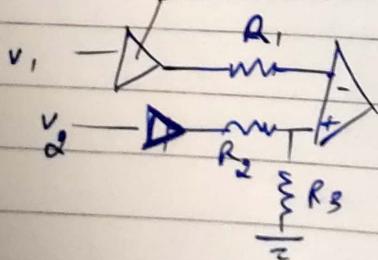


▷ Buffer Non-inverting op-amp

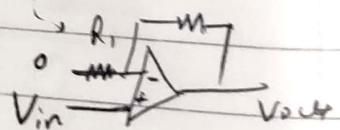

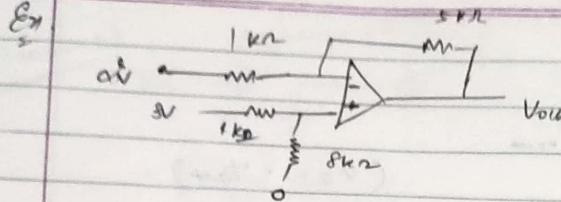

(Q2)
Simplification

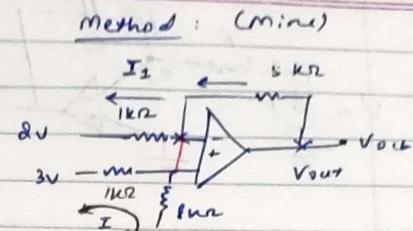

$$\frac{3}{9} k\Omega = I \quad V_x = \frac{3 \cdot 8}{9} = \frac{8}{3} V$$



$$\frac{8}{3} = 2 + (I_0)(10^3 \Omega)$$

$$I_0 = \frac{2}{3} \text{ mA}$$

$$\cancel{V_{out}} = \frac{8}{3} \text{ mA} = I = \frac{2}{3} \text{ mA}$$

5

$$\boxed{\frac{18}{3} = V_{out} = 6V}$$

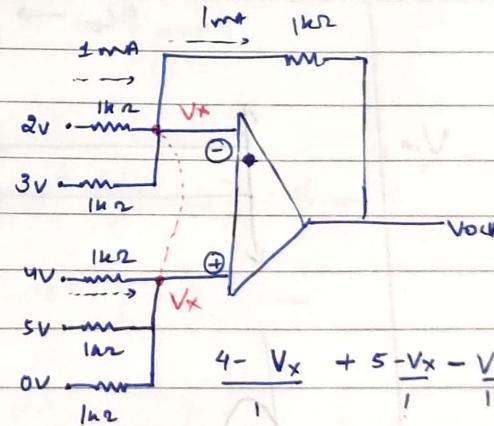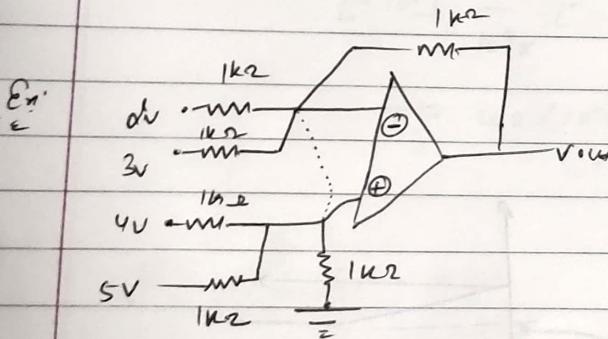


$$\frac{V_x - V_{out}}{1} = 1$$

$$\boxed{V_x = 3V}$$

$$\boxed{V_{out} = 2V}$$

Op amp as Integrator.

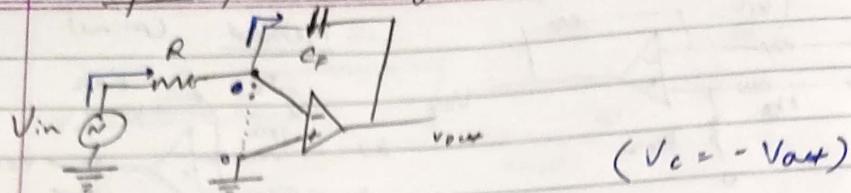

$$\frac{V_{in}}{R} = IR \quad i = \frac{dQ}{dt} = C \frac{dV}{dt}$$



$$\frac{V_{in}}{R} = I_{Cf} = -C \frac{dV_{out}}{dt}$$

$$-\int \frac{V_{in}}{R} dt = \int dV_{out} = V_{out}$$

$$\frac{-1}{Rc} \int V_{in} dt = V_{out}(t)$$

area under $V_{in}-t$ curve / Rc

also: $\frac{1}{Rc} \rightarrow$ time

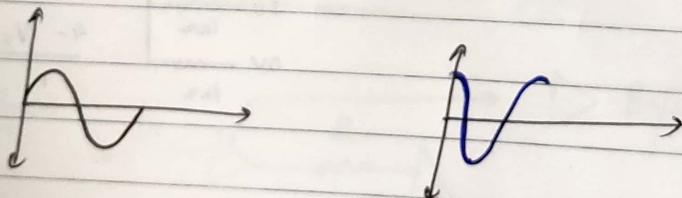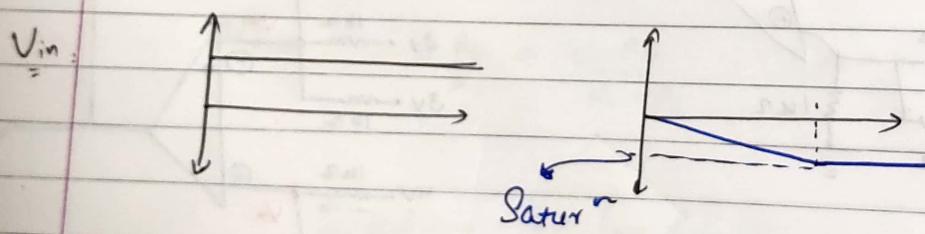


$$X_C = \frac{1}{\omega_C} = \frac{1}{2\pi f_C}$$

$$V_{out} = -\frac{X_C}{R} \cdot V_{in}$$

$$Av = -\frac{X_C}{R} = \frac{1}{2\pi \cdot R \cdot C \cdot f}$$

of:

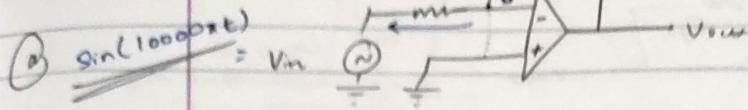

$$\checkmark \left(-\frac{V_{in}}{s} \right) mA + I_i$$

$$\checkmark \underline{V_{out} = 0} = V_C = V_R = i_R \cdot 100 \text{ k}\Omega$$

$$[i_R = \frac{V_{out}}{100}]$$

$$I_i - I_R = I_C = C \cdot \frac{dV_C}{dt} = \left[-V_{in} - \frac{V_{out}}{100} \right] \text{ mA} = 10^{-8} \cdot \frac{dV_{out}}{dt}$$


$$\int -V_{in} \cdot 10^5 dt - \int V_{out} \cdot 10^3 dt = \int dV_{out} = \frac{dV_{out}}{dt}$$

$$\Rightarrow (-10^5) \int V_{in} dt + (-10^3) \int V_{out} dt = \int dV_{out}$$

$$[-10^5] \cdot \frac{1}{10^4 \pi} \left[-\cos [10^4 \pi t] \right]_0^t \approx V_{out}$$

$$+ \frac{10}{\pi} \cos (10^4 \pi t) \Big|_0^t \approx V_{out}$$

(b)

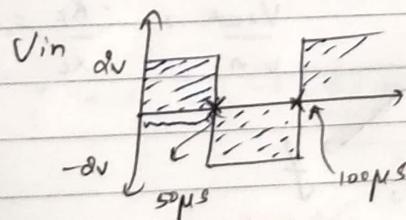


$$-10^5 \left[\int V_{in} dt \right] = V_{out}$$


$$-10^5 \cdot [10^{-4}] \rightarrow$$

$$\text{Area } B_1: 2 \times 50 \times 10^{-6}$$

$$= 10^{-4}$$

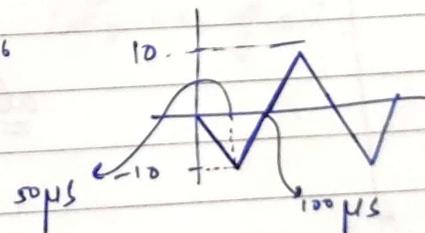

Op-Amp as Differentiator

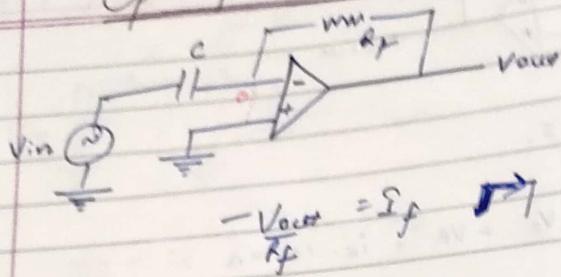

$$-\frac{V_{out}}{R_F} = I_C \rightarrow$$

$$C \frac{d(+Vin)}{dt} = I_C \rightarrow$$

$$\frac{C}{\epsilon} \frac{d(Vin)}{dt} = -\frac{V_{out}}{R_F}$$

$$\boxed{-\frac{C}{\epsilon} \frac{d(Vin)}{dt} = V_{out}}$$

\neq Vin: $A \sin(\omega t)$


$$V_{out} : [\omega CR_F \cos \omega t = V_{out}]$$

$$X_C = \frac{1}{\omega f_C}$$



$$V_{out} = -\frac{R_F}{X_C} \cdot V_{in}$$

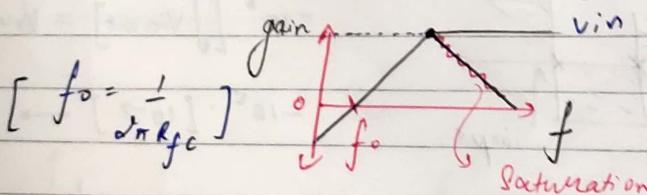
$$\frac{V_{out}}{V_{in}} = -\frac{R_F}{X_C} = A = -R_F \cdot f_C$$



$$\text{also } Z_{in} = X_C \uparrow \downarrow$$

$$\downarrow Z_{in} \uparrow X_C \uparrow \downarrow \uparrow \text{(Problem)}$$

Solution
to
2

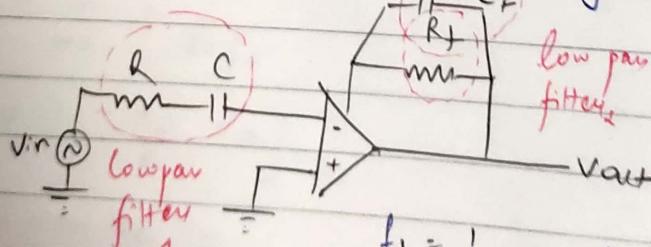


$$Z_{in} = \sqrt{R^2 + X_C^2}$$


$$[Z_{in} = R] \Leftrightarrow \text{better}$$

$$f_1 = \frac{1}{2\pi R_C}$$

$$f_2 = \frac{1}{2\pi R_C f_F}$$

$$f_2 > f_1$$

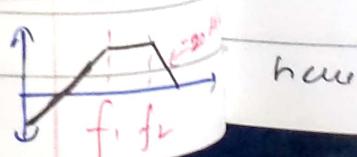

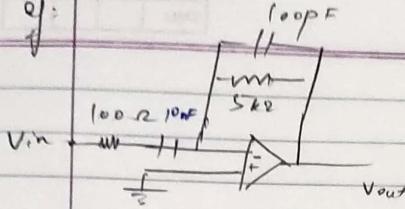

Page No. _____
Date _____

$$f_1 = \frac{1}{2\pi C(D-\theta)(100)} = \frac{1}{2\pi CR} = \frac{10^6}{2\pi}$$

$$f_2 = \frac{1}{2\pi \cdot 10^{-10} \cdot 5 \times 10^3} = \frac{10^6}{\pi}$$

$$f_s < [f_1 < f_2]$$

for accurate diff: $f_{f_0} \rightarrow \left[\frac{10^5}{2\pi} = f_s \right]$

Q:
if $V_{in} = A \sin(\omega t + 3000t)$

$$3 \times 10^3 \ll f_2 \approx \frac{10^6}{2\pi} \quad \checkmark$$

then

$$(RL) 4\pi \cdot (3000) \cos(6000\pi t) - V_{out}$$

$$10^{-6} (12 \times 10^3) \pi \cos(6000\pi t)$$

This $-RL \frac{dV_{in}}{dt} = V_{out}$ is app. if only

~~if~~ \ll ~~if~~ ?

[Slew rate: $\frac{V_{max} - V_{min}}{\text{time taken}}$]
(min)

[$f_s \ll f_2$]

how $f \in [0, f_1]$ generally $[f_s = \frac{f_1}{10}]$