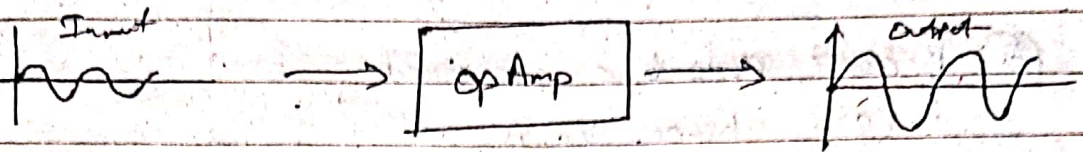


25th Jan 2022

Date
DELTA Pg No.

Operational Amplifier (Opamp)



- * It is a very high gain differential amplifier with high input impedance and low output impedance.
- * Could be used for performing ~~add~~ add, sub, mul, div, integration, diff. etc. Hence called Operational Amplifier.


Circuit Symbol :-

$V_1, V_2 \rightarrow$ Input

$V_{out} \rightarrow$ Output

$V^+, V^- \rightarrow$ Biasing

$$V_{out} = A(V_1 - V_2)$$

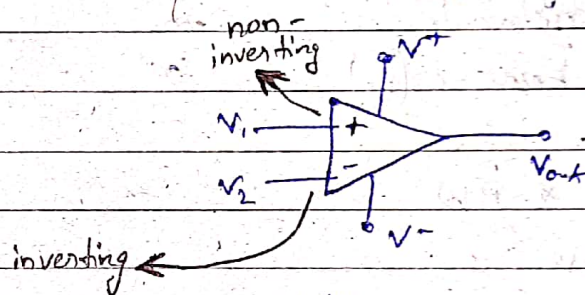

the difference b/w V_1 and V_2 gets amplified.


where A is open loop gain of op-amp (without feedback).

① If $V_2 = 0$

$$V_{out} = A(V_1 - V_2)$$

$$= AV_1 \rightarrow \text{this non inverting}$$

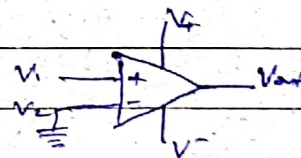($\because V_2$ is generally grounded $\Rightarrow V_2 = 0$)



②

$V_2 \neq 0, V_1 = 0$

$$V_{out} = A(V_1 - V_2)$$


$$= -AV_2 \text{ (inverted)}$$

as input output

180° phase shift

as input output \Rightarrow inverted

(2)

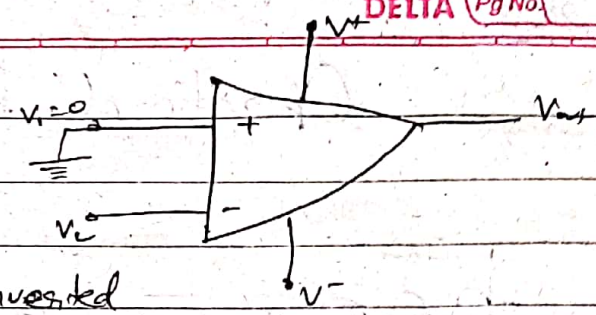

⊗ Because output is inverted in (2), hence V_2 is called inverted ~~in~~ terminal.

Characteristic of OpAmp:-

<u>Char</u>	<u>Ideal</u>	<u>Practical</u>
① Voltage gain, (A_v)	∞	$10^5 - 10^6$
② Input Resistance, (R_i)	∞	$1M\Omega$
③ Output Resistance, (R_o)	0	$10 - 100\Omega$
④ ⊗ Gain \times BW	∞	$10^6 Hz$
⑤ BW	∞	$10^6 Hz$ (gain = 1)
⑥ CMRR (common mode rejection ratio)	∞	10^6
⑦ Slew rate	∞	$80 \frac{V}{\mu sec}$ ($\frac{V}{\mu sec}$)


Gain \uparrow BW \downarrow
 and
 BW \uparrow Gain \downarrow


$$V_1 - V_2 = V_d$$

$$A = 10^5$$

$$V_d = 1mV$$

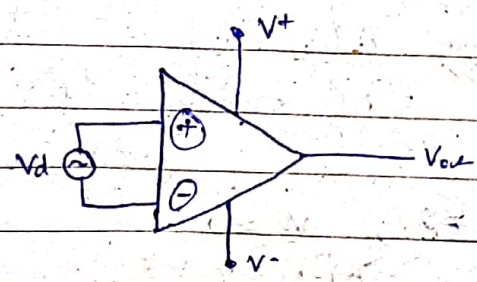
$$V_{out} = A \times V_d = 10^5 \times 1mV = \boxed{100V}$$



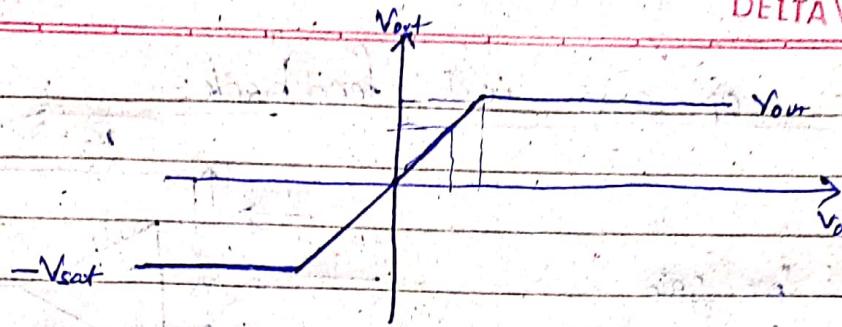

~~Vout~~

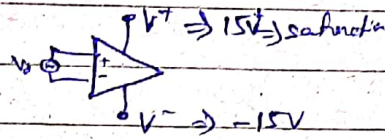Vsaturation \Rightarrow decided by the Biasing.




$\Rightarrow V_{out} = +15V$

(*) V_{out} can never be ~~in~~ above than Vsaturation i.e. Biasing voltage.

Common mode Operation :-

\rightarrow Results in 0 output (ideally).

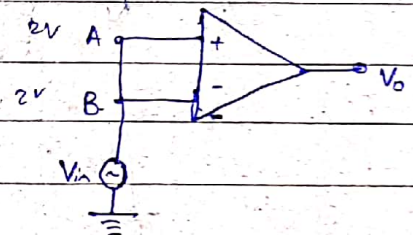\Rightarrow Amplify the difference signal while neglecting the common signal out the two inputs.



\Rightarrow Noise is generally common to both inputs (A and B), hence will get neglected.

\rightarrow common signal
 $C + B_1 \Rightarrow$ at A
 $C + B_2 \Rightarrow$ at B

$$\begin{aligned} V_{out} (\text{Amplified}) &= C + B_1 - C - B_2 \\ &= (B_1 - B_2) \end{aligned}$$

(*) Hence the common signal neglected.

Basic op-amp with feedback:-


closed loop gain

$$G = \frac{V_{out}}{V_I}$$

$$V_{out} G = A (V_2 - V_1)$$

$$V_2 - V_1 = \frac{V_{out}}{A} \approx 0$$

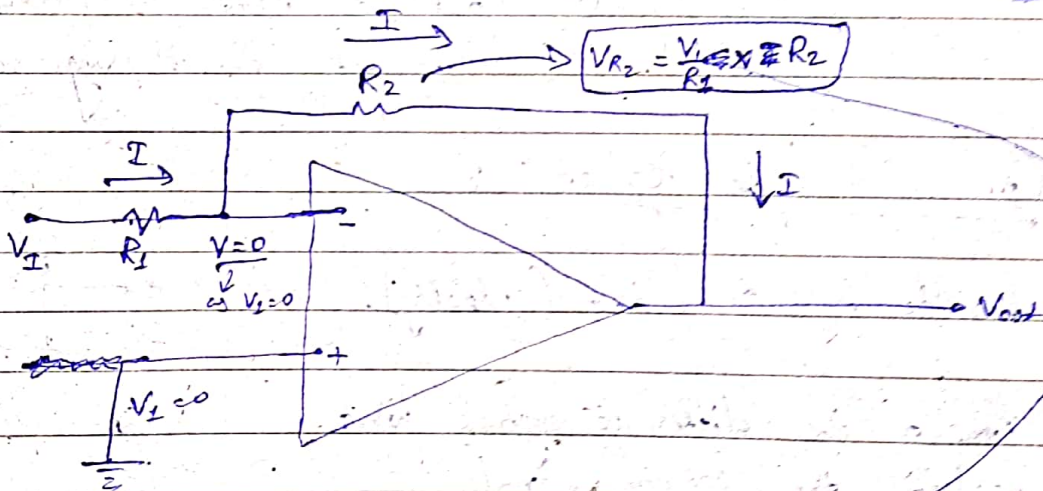$\therefore V_2 = V_1 \Rightarrow$ virtually short circuit b/w input terminals and $V_1 = 0$ (as grounded), $\therefore V_2 = V_1 = 0$



$$I_1 = \frac{V_I - 0}{R_1} = \frac{V_I}{R_1}$$

By KVL,

$$V_{out} = - \left(\frac{V_I}{R_1} \times R_2 \right)$$

$$\frac{V_{out}}{V_I} = - \left(\frac{R_2}{R_1} \right)$$

\rightarrow gain (closed loop) (inverted)

\rightarrow as V_{out} is (-ve).