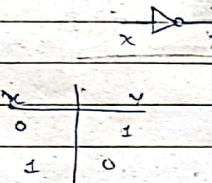
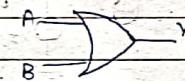


UNIT - 5

SEM)

Boolean AlgebraNOT (A' , \bar{A})OR ($Y = A + B$)

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

$A + A = A$
 $A + 1 = 1$
 $A + 0 = A$
 $A + \bar{A} = 1$

$$\begin{aligned}
 & \cancel{AB + A\bar{B}} \\
 &= A(B + \bar{B}) \\
 &= A(1) \\
 &= A
 \end{aligned}$$

AND ($A \cdot B$)

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

$$\begin{aligned}
 A \cdot A &= A \\
 A \cdot 1 &= A \\
 A \cdot 0 &= 0
 \end{aligned}$$

$$A \cdot \bar{A} = 0$$

$$\begin{aligned}
 & AB + A\bar{B} + A\bar{B}\bar{C} \\
 &= AB + A\bar{B}(C + \bar{C}) \\
 &= \cancel{AB} AB + AB \\
 &= A(B + \bar{B}) \\
 &= A
 \end{aligned}$$

$$AB + A\bar{B} + A\bar{B}\bar{C}$$

Q. $(A+B)(A+C)$ minimize the expression.

$$\begin{aligned}
 & AB + A\bar{B} + A\bar{B} \\
 \Rightarrow & A(B + \bar{B}) + A\bar{B} \\
 \Rightarrow & A + \bar{A}\bar{B} \\
 \cancel{1} \leftarrow & = (A + \bar{A})(A + \bar{B}) \\
 &= (A + \bar{B})
 \end{aligned}$$

$$\begin{aligned}
 & AB + A\bar{B} + A\bar{B} \\
 &= B(A + \bar{A}) + A\bar{B} \\
 &= B + A\bar{B} \\
 &= (B + \bar{B})(B + A) \\
 \cancel{1} \downarrow & \\
 \cancel{AM:} \Rightarrow & B + A
 \end{aligned}$$

$$\begin{aligned}
 & AB + A\bar{B} + BC \\
 &= AB + AC + BC(A + \bar{A}) \\
 &= AB + \bar{A}C + ABC + \bar{A}BC \\
 &= AB(1 + C) + \bar{A}C(B + 1) \\
 &= AB + \bar{A}C
 \end{aligned}$$

comparing we get
that BC is of no use
in question

Hence $BC \Rightarrow$ redundant term

Property

$$\begin{aligned}
 A + AB &= (A+A)(A+B) \\
 &= 1(A+B) \\
 &= (A+B)
 \end{aligned}$$

DeMorgan's Theorem

$$\overline{A \cdot B \cdot C} = \overline{A} + \overline{B} + \overline{C}$$

$$\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

Minimization

SOP
 (Sum of Product)
 generally used

$$\text{eg. } ABC + ABD + AC$$

minimal canonical

POS
 (Product of Sum)

$$\text{eg. } (A+B+C)(A+C)(C+D)$$

minimal canonical

$$Q. AB + A\bar{B}\bar{C} + A\bar{B}\bar{C}\bar{D}$$

$$AB\bar{C} + A\bar{B}(1 + \bar{C}\bar{D})$$

①

$$= A\bar{B}\bar{C} + A\bar{B}$$

$$= A(\bar{B}\bar{C} + \bar{B})$$

$$= A(\bar{B} + B)(\bar{B} + \bar{C}) = A(\bar{B} + \bar{C}) = A\bar{B} + A\bar{C}$$

$$Q. (A+B)(A+C)$$

$$= A \cdot A + A \cdot C + B \cdot A + B \cdot C$$

$$= A + A(C + B) + BC$$

$$= A(1 + (B+C)) + BC$$

①

$$\cancel{A}M = A + BC$$

Q. Minimize the expression using SOP.

Sol. SOP form is used when output of logical expression is 1.

$$\begin{aligned} Y &= \bar{A}\bar{B} + A\bar{B} \\ &= \bar{B}(\bar{A} + A) \\ &= \bar{B} \end{aligned}$$

0 0	1
0 1	0
1 0	1
1 1	0

(a) $Y = \sum m(0, 2)$ \Rightarrow $\begin{array}{l} 00 \rightarrow 0 \\ 01 \rightarrow 1 \\ 10 \rightarrow 2 \\ 11 \rightarrow 3 \end{array} \Rightarrow \bar{A}\bar{B}$

Y is 1 at 0 and 2. $\Rightarrow \bar{A}\bar{B} + A\bar{B}$

$Y = \sum m(0, 2, 3)$

A - B	Y
0 0	1
0 1	0
1 0	1
1 1	1

 $\Rightarrow Y = \bar{A}\bar{B} + A\bar{B} + AB$

Q. Expression in SOP form.

Sol. $Y = \bar{A}\bar{B} + A\bar{B} + AB$

$$\begin{aligned} &= \bar{B}(\bar{A} + A) + AB \\ &= \bar{B} + AB \\ &= (\bar{B} + A)(\bar{B} + B) \\ &= \bar{B} + A \\ &= \underline{A + \bar{B}} \quad AM \end{aligned}$$

SOP \Rightarrow consider 0
POS \Rightarrow consider 1

SOP

Date /
DELTA Pg NO.

Minimal
form

Canonical
forms

$$\text{Eg. } A + AB + A\bar{B}C + CA$$

$$\text{eg. } AB + BCA + CD$$

↓
no definite no. of
variables in an expression

$$\text{Eg. } A\bar{B}C + B\bar{C}A + C\bar{A}B$$

$$\text{eg. } AB + BC + CB + AA$$

$$\text{eg. } ABC + BCA + CAB$$

(*) each term has same no.
of variables
and all variables included

C. Convert into canonical

$$A + \bar{B}C$$

SOP

$$= A(B + \bar{B})(C + \bar{C}) + \bar{B}C(A + \bar{A})$$

$$= (AB + A\bar{B})(C + \bar{C}) + A\bar{B}C + \bar{A}\bar{B}C$$

$$= ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}C$$

POS form (Product of Sums)

⇒ look for zero (0).

C.

$$A + B \mid Y$$

$$0 \ 0 \mid 1$$

$$0 \ 1 \mid 0 \quad \Rightarrow \ A + B$$

$$1 \ 0 \mid 1$$

$$1 \ 1 \mid 0 \quad \Rightarrow \ \bar{A} + \bar{B}$$

$$Y = (A + \bar{B})(\bar{A} + \bar{B}) = A\bar{A} + A\bar{B} + \bar{B}\bar{A} + \bar{B}\bar{B} +$$

$$= 0 + A\bar{B} + \bar{B} + \bar{A}\bar{B}$$

$$= \bar{B} \underbrace{(A + 1 + \bar{A})}_{(1) \text{ as there is } 1} = \bar{B}$$

KMap

SOP \Rightarrow consider 0
POS \Rightarrow consider 1

Date /
DELTA Pg No.

$$\Sigma_m(0, 2) = \Pi M(1, 3)$$

for SOP

for POS

$$F(A, B, C) = \Sigma_m(0, 1, 4, 7) = \Pi M(2, 3, 5, 6)$$

A B C

$$1 - 0 - \bar{A}\bar{B}\bar{C} \leftarrow 0 - 0 - 0 - (1)$$

$$1 - 0 - \bar{A}\bar{B}C \leftarrow 1 - 0 - 0 - (1)$$

$$2 - 0 - 1 \bar{0}$$

$$2 - 0 - 1 \bar{1} \quad (1)$$

$$2 - 1 - 0 \bar{0}$$

$$2 - 1 - 0 \bar{1} \quad (1)$$

$$B - 1 - 1 \bar{0}$$

$$B - 1 - 1 \bar{1} \quad (1)$$

By SOP,

$$\Rightarrow Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C}$$

$$+ ABC$$

By POS,

$$Y =$$

$$2 \Rightarrow 010 \rightarrow 0 \Rightarrow A + \bar{B} + C$$

$$3 \Rightarrow 011 \rightarrow 0 \Rightarrow A + \bar{B} + \bar{C}$$

$$5 \Rightarrow 101 \rightarrow 0 \Rightarrow \bar{A} + B + \bar{C}$$

$$6 \Rightarrow 110 \rightarrow 0 \Rightarrow \bar{A} + \bar{B} + \bar{C}$$

0 0 0 0	0 0 0 1	0 0 1 0	0 0 1 1	0 + 0 0
0 0 1 0	0 0 1 1	0 1 0 0	0 1 0 1	0 + 0 1
0 1 1 0	0 1 1 1	0 1 0 0	0 1 0 1	0 + 1 0
0 1 0 1	0 1 0 1	0 1 1 0	0 1 1 1	0 + 1 1
0 1 0 0	0 1 0 0	1 0 0 0	1 0 0 1	1 0 0 0
1 0 1 0	1 0 1 1	1 0 1 0	1 0 1 1	1 0 1 0
1 0 1 1	1 0 1 1	1 1 0 0	1 1 0 1	1 0 1 1
1 1 0 0	1 1 0 1	1 1 0 1	1 1 1 0	1 1 0 0
1 1 0 1	1 1 1 0	1 1 1 0	1 1 1 1	1 1 1 1

Product of
all Mors.

same as 1st
canonical
form.

Dual Expression:

(1) AND (\cdot) \leftrightarrow OR (+)

(2) 1 \leftrightarrow 0

(3) Keep the variable as it is.

Q. Find Dual.

$$ABC + \bar{A}BC + ABC$$

$$\Leftrightarrow (A+B+\bar{C}) \cdot (\bar{A}+B+C) \cdot (A+\bar{B}+C)$$

Complement Expression:

(A) AND \leftrightarrow OR

\cdot \leftrightarrow +

(B) 1 \leftrightarrow 0

(C) Complement of each variable

Eg. Find the complement

$$Y = ABC + \bar{A}BC + A\bar{B}C$$

$$\bar{Y} = (\bar{A}+\bar{B}+\bar{C}) \cdot (A+\bar{B}+\bar{C}) \cdot (\bar{A}+B+\bar{C})$$

Basic Building Blocks:

NOT
AND
OR } \rightarrow Basic gate

NAND
NOR } \rightarrow Universal gates


EXOR
EXNOR } \rightarrow Arithmetic gate

NAND Gate :-

AND + NOT



A B Y

0 0	1
0 1	0
1 0	0
1 1	0

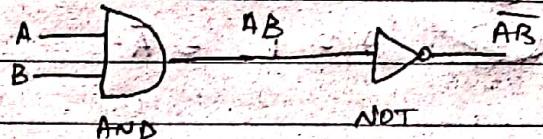

OR + NOT

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

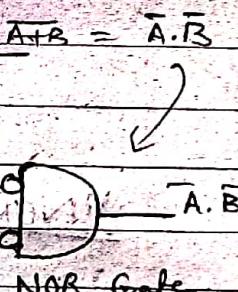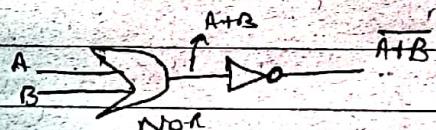

EXOR or XOR :-

(Exclusive OR)

$$Y = A \oplus B$$

$$= A\bar{B} + \bar{A}B$$

$$= \bar{A}B + A\bar{B}$$



$$Y = A \oplus B = A\bar{B} + \bar{A}B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

When A = B, Output is 0. When A ≠ B, Output 1.

$$\textcircled{5} \quad A \oplus A = 0$$

$$\textcircled{13} \quad A \oplus \bar{A} = 1$$

$$\textcircled{B} \quad A + 0 = A$$

$$\cancel{A \oplus I} = \bar{A}$$

$$Q. A \oplus A \oplus A = A$$

$$\underline{80} \quad \Rightarrow -0 + A = 1$$


$$\textcircled{8}, \quad A \oplus A \oplus A \oplus A$$

The diagram consists of three horizontal wavy lines. The bottom line is labeled 'A' at its center. Above it is a longer wavy line labeled 'B' at its center. The top line is the shortest wavy line labeled 'C' at its center.

$$= 0$$

$$\textcircled{A} \quad \textcircled{B} \quad A \oplus A \oplus A \oplus \dots \underset{n}{=} A \rightarrow \begin{cases} \text{if } n = \text{odd} \\ = 0, \quad \text{if } n = \text{even} \end{cases}$$

XNOR :-

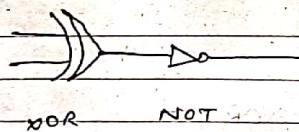

$$Y = A \odot B = AB + \bar{A}\bar{B}$$



A	B		C
0	0		1
0	1		0
1	0		0

$\text{AOA} = \cdot$

$$A = B \Rightarrow \text{output} = 1$$

$$A \neq B \Rightarrow \text{output} = 0$$

$$\underline{A \odot A = 1}$$

$$A \odot A \odot A = ?$$

$$AOA\ominus AOA = ?$$