
 



## • Pairs

 

## • Quads



## • Octets

 


Sum of two quads

$$A\bar{c} + Ac = A(\bar{c}+c)$$

obtain


- Example: Simplified expression for Boolean function  $Y$  using Karnaugh's map shown:

K-map for  
function  $Y$

 


$$\therefore Y = \bar{A}\bar{B}D + A\bar{C} + C\bar{D}$$

- Overlapping Groups:

 

$$\therefore Y = A + B\bar{C}D$$

- Rolling the map:


 


$$Y = B\bar{D}$$

$$\begin{aligned} Y &= B\bar{C}\bar{D} + B\bar{C}D \\ &= B\bar{D}(\bar{C} + C) \\ &= B\bar{D} \end{aligned}$$



  
- More examples: Find  $Y$  by simplifying the K-maps shown



$$\therefore Y = \bar{C} + \bar{A}D + A\bar{B}\bar{D}$$


$$\text{or } Y = \bar{C} + \bar{A}D + \bar{B}D$$

- Eliminating redundant groups:

 

The quad is redundant as all its 1's have been included in 4 'pairs'.

 - Example: Simplify  $Y = F(A, B, C, D) = \sum m(7, 9, 10, 11, 12, 13, 14, 15)$



$$Y = AB + AC + AD + BCD$$

• Don't Care conditions :

In some digital circuits, certain combinations of inputs are needed or are of no consequence to the desired outputs, these are called don't care conditions and are marked as 'x' in the truth table. This 'x' can be taken as either 0 or 1 depending upon which way it leads to a simplified Boolean function.

Example :

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	x
1	0	1	1	x
1	1	0	0	x
1	1	0	1	x
1	1	1	0	x
1	1	1	1	x

K-map

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	0	0	0	0
$AB$	x	x	x	x
$A\bar{B}$	0	1	x	x

$$\therefore Y = AD$$

(Otherwise, it would have been  $Y = A\bar{B}\bar{C}D$ )

all 'x' are don't care conditions


• Example : Give the simplest circuit to implement the following function:  
 $Y = F(A, B, C, D) = \sum m(7) + d(10, 11, 12, 13, 14, 15)$

	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	3	2
$\bar{A}B$	4	5	7	6
$AB$	12	13	15	14
$A\bar{B}$	8	9	11	10

K-map of function Y


If we combine one 'x' with '1' and make a pair then  $Y = BCD$

 (Otherwise Y would have been  $\bar{A}BCD$ )





## 10. Half adder

 

Truth Table

A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$= \bar{A}B + A\bar{B} \therefore \text{SUM} = \bar{A}B + A\bar{B} = A \oplus B$$

$$\text{CARRY} = A.B$$

(C<sub>0</sub>)

## 11. Full-adder

Truth table

A	B	C <sub>0</sub>	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$\text{SUM} = \bar{A}\bar{B}C_0 + \bar{A}B\bar{C}_0 + \bar{A}B\bar{C}_0 + ABC_0$$

$$\text{CARRY} = \bar{A}BC_0 + A\bar{B}C_0 + AB\bar{C}_0 + ABC_0$$


$$\begin{aligned} \text{SUM} &= C_0 [\underbrace{\bar{A}\bar{B} + A\bar{B}}_{\text{ex-NOR}}] + \bar{C}_0 [\underbrace{\bar{A}B + AB}_{\text{ex-OR}}] \\ &= C_0 \bar{D} + \bar{C}_0 D \quad \text{assume } D \\ &= C_0 \oplus D \\ &= C_0 \oplus (A \oplus B) \end{aligned}$$

$$\text{CARRY} = (\bar{A}B + A\bar{B})C_0 + AB(C_0 + \bar{C}_0)$$


$$= \bar{A}BC_0 + A\bar{B}C_0 + AB$$

$$= AB + BC_0 + AC_0 \quad (\text{use Karnaugh's map})$$

See next page K-map

 

## K-MAP for CARRY

 


$\therefore \text{CARRY} = AB + BC_0 + AC_0$


Problem : Realise  $Y = A.B + \bar{C}$  using only one types of gates .

WE can use only universal gate ie NOR or NAND to make circuits with only 1 gate

Method 1 Using NOR gates only :

 

Method 2 Using NAND gates only :

 


Method 3

$$Y = A.B + \bar{C}$$

$$= \overline{\overline{A.B + \bar{C}}}$$

$$= \overline{(A.B) \cdot C}$$

 

Note : The last circuit can be obtained from second one by removing cascades of two-NOT-gates one after the other which are redundant !

Method 4 :

$$Y = A.B + \bar{C} = \overline{\overline{A.B + \bar{C}}} = \overline{\overline{A.B} \cdot C} = \overline{(\overline{A+B}) \cdot C} = \overline{(\overline{A+B})} + \bar{C} = \overline{\overline{A+B}} + (\bar{C})$$

Circuit resulting from this expression would be same as in method 1 .



### 13. Sequential circuits: Flip flops (FF)

- A flip flop is a circuit called 'bistable' (having two stable states)


- A flip flop has memory, storing one bit information

When flip flop has its output as HIGH ( $\approx +V_{cc} = +5V$ ) it stores '1'


When flip flop has its output as LOW ( $\approx 0V$ ), it stores '0'.

- A flip flop has 'feedback' connections.

 - SR flip-flop: This is a SR latch (Basic storage element) using NOR gate



outputs  $\Rightarrow$

 

NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

('R' stands for reset; 'S' stands for setting)

↓  
making  
output  
'0'

↓  
making  
output  
'1'

Truth table

R	S	$Q_{n+1}$
0	0	$Q_n$
0	1	1
1	0	0
1	1	? (forbidden)

next state


previous  
state

'set' to '1'

'reset' to '0'

indeterminate

 Same circuit can also be realised  
by NAND gates:



NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

This circuit too  
is characterised by  
the same  
truth table.  
(Verify yourself!)



R	S	$Q_n$	$\overline{Q_n}$	$Q_{n+1}$	$\overline{Q_{n+1}}$
---	---	-------	------------------	-----------	----------------------

0	0	0	1	0	1
---	---	---	---	---	---

0	0	1	0	1	0
---	---	---	---	---	---

$Q_{n+1} = Q_n$

1	0	0	1		
---	---	---	---	--	--

$Q_{n+1} = 0$

1	0	1	0		
---	---	---	---	--	--

0	1	0	1		
---	---	---	---	--	--

$Q_{n+1} = 1$

0	1	1	1		
---	---	---	---	--	--

1	1	0	1		
---	---	---	---	--	--

1	1	1	0		
---	---	---	---	--	--

$Q_{n+1}$  and  $\overline{Q_{n+1}}$   
don't remain  
complementary

(Not in order!)


• Clocked SR flip flop: (with enable)

AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

If  
A = 1 (fixed)

then  
 $Y = A \cdot B = B$

 

Truth table


EN	S	R	$Q_{n+1}$
1	0	0	$Q_n$
1	1	0	1
1	0	1	0
1	1	1	?
0	x	x	$Q_n$

no change  
(previous state  
continues)

forbidden

no change  
(previous state  
continues)

• D flip flop:

 

↓ D

R	S	$Q_{n+1}$
0	0	$Q_n$
0	1	1
1	0	0
1	1	? ?

Truth Table


EN	D	$Q_{n+1}$
0	x	$Q_n$
1	0	0
1	1	1

last state

reset  
set



## • Jk Flip flop:

 


J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\overline{Q_n}$

J	k	$Q_n$	$Q_{n+1}$
1	1	0	1
1	1	1	0

$$\therefore Q_{n+1} = \overline{Q_n}$$

$$\therefore Q_{n+1} = \overline{Q_n}$$

## • Toggle Flip flop (T flip-flop)

 

$ck = 1$

T	$Q_{n+1}$
0	$Q_n$
1	$\overline{Q_n}$

On appearance of each '1' at the input, the output would 'toggle' (becoming '1' from '0' or becoming '0' from '1').